

# **SRM VALLIAMMAI ENGINEERING COLLEGE**

(An Autonomous Institution)

SRM Nagar, Kattankulathur – 603 203

## **DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING**

### **QUESTION BANK**



### **IV SEMESTER**

**B.E – MEDICAL ELECTRONICS**

**1905408 -ELECTRICAL ENGINEERING**

**Regulations – 2019**

**Academic Year 2021 – 2022**

*Prepared by*

**Ms. R.Elavarasi - Assistant Professor/EEE**



# SRM VALLIAMMAI ENGINEERING COLLEGE

SRM Nagar, Kattankulathur – 603 203.







DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING





## QUESTION BANK








**SUBJECT : 1905408 ELECTRICAL ENGINEERING**





**SEM /YEAR : IV / II**


<b><u>UNIT I - ELECTRICAL CIRCUITS AND ANALYSIS</u></b>			
Ohms law, DC and AC circuits fundamentals, Energy sources, Kirchhoff's laws, Mesh and Nodal analysis, Star -delta and Delta -star transformation; theorems and simple problems : Superposition, Thevenin 's, Maximum power transfer theorem.			
<b>PART-A</b>			
<b>S.No</b>	<b>Questions</b>	<b>BT Level</b>	<b>Competence</b>
1.	State kirchhoff's laws.	BTL 3	Apply
2.	Mention the limitations of ohm's law.	BTL 3	Apply
3.	List out the examples for active & passive elements.	BTL 1	Remember
4.	Give a relation of line and phase values in star and delta connections.	BTL 2	Understand
5.	Define node and mesh.	BTL 3	Apply
6.	Two resistances of $4\Omega$ and $6\Omega$ are connected in parallel across 10V battery. Calculate the current through $6\Omega$ resistance.	BTL 1	Remember
7.	Write the formula for form factor and peak factor.	BTL 1	Remember
8.	Examine current division rule and voltage division rule.	BTL 2	Understand
9.	Define the term power factor.	BTL 1	Remember
10.	Write the expression for equivalent resistance when two resistors are connected in parallel.	BTL 4	Analyze
11.	Classify the energy sources.	BTL 4	Analyze
12.	Draw the symbol for dependent and Independent current source.	BTL 1	Remember
13.	How to convert voltage source to current source.	BTL 4	Analyze
14.	Compare Series and Parallel Circuits	BTL 5	Evaluate
15.	What do you mean by thevenin's theorem?	BTL 6	Create
16.	Sketch the equivalent circuit of Thevenin theorem.	BTL 5	Evaluate
17.	Define superposition theorem.	BTL 6	Create
18.	Express the formula to find the load current in thevenin theorem.	BTL 2	Understand
19.	Write the condition to obtain maximum power in maximum power transfer theorem?	BTL 1	Remember
20.	State superposition theorem.	BTL 2	Understand
<b>PART-B</b>			

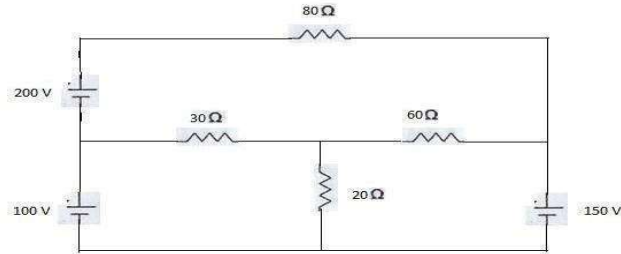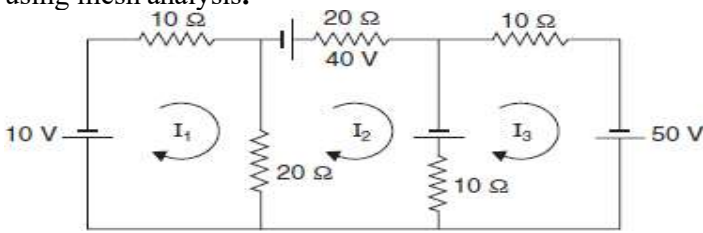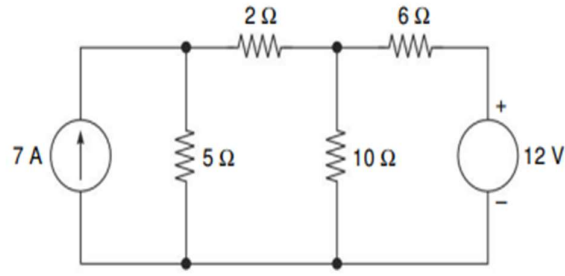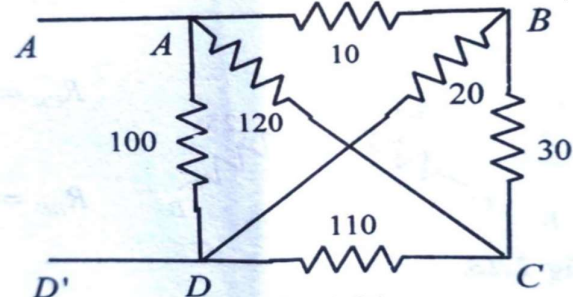1.	<p>Estimate the current through the Various branches in the circuit of the following figure. Using mesh analysis. (13)</p> 	BTL 4	Analyze
2.	<p>Identify the currents <math>I_1</math>, <math>I_2</math> and <math>I_3</math> in the network shown in Fig. using mesh analysis. (13)</p> 	BTL 4	Analyze
3.	<p>For the circuit shown, find the nodal voltages and the current through the <math>2\Omega</math> resistance. (13)</p> 	BTL 1	Remember
4.	<p>Find the equivalent resistance between A and B for the circuit given below. (13)</p> 	BTL 3	Apply
5.	<p>Evaluate the equivalent resistance of the circuit using star – delta conversion. (13)</p>	BTL 1	Remember

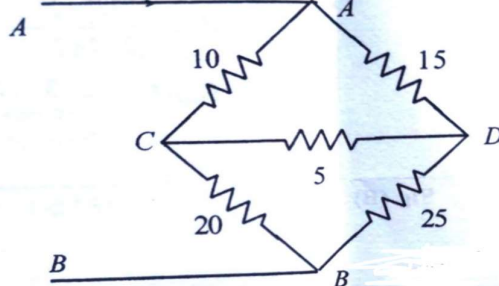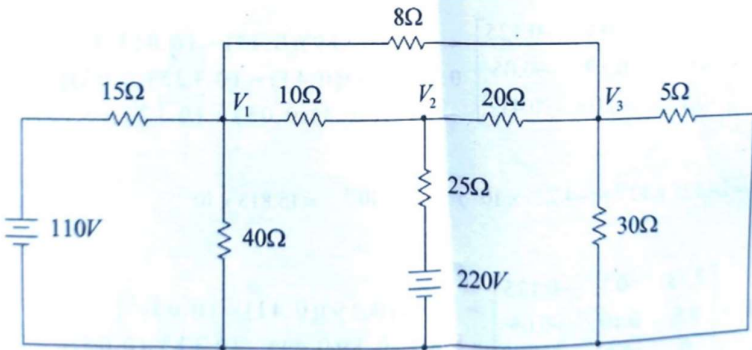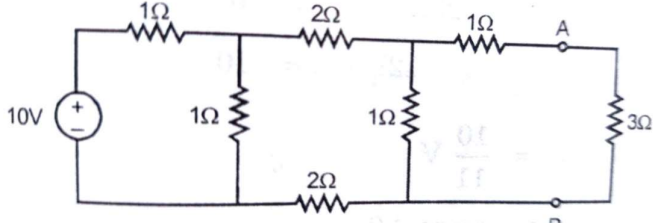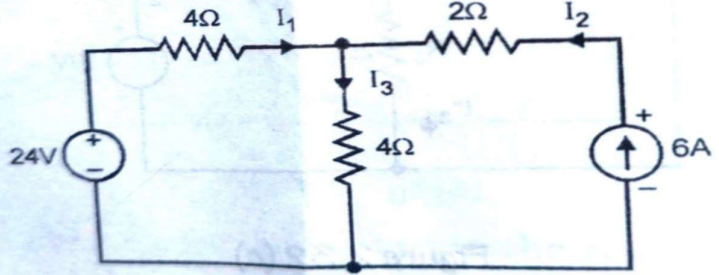			
6.	<p>Solve the problem given below using nodal analysis and find the node voltages <math>V_1</math>, <math>V_2</math>, <math>V_3</math>. (13)</p> 	BTL 4	Analyze
7.	<p>Derive an expression for Equivalent resistance of Star to Delta and Delta to Star transformation. (13)</p>	BTL 2	Understand
8.	<p>Find Thevenin's equivalent voltage across the terminal AB and also find the current through <math>3\Omega</math> resistor as shown in figure (13)</p> 	BTL 1	Remember
9.	<p>Using Super position theorem find the current through various branches. (13)</p> 	BTL 1	Remember
10.	<p>Write the statement for thevenins theorem and also bring out the steps to be followed to draw thevenins equivalent circuit? (13)</p>	BTL 2	Understand
11.	<p>Draw the Thevenin's equivalent circuits across the terminal AB for the given network. (13)</p>	BTL 2	Understand

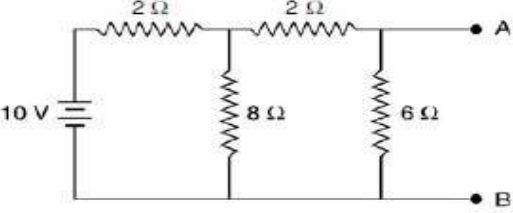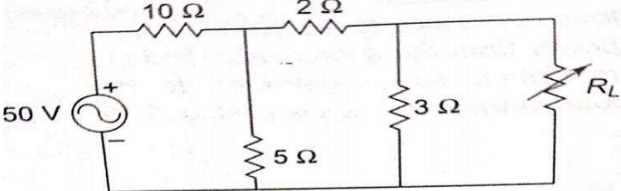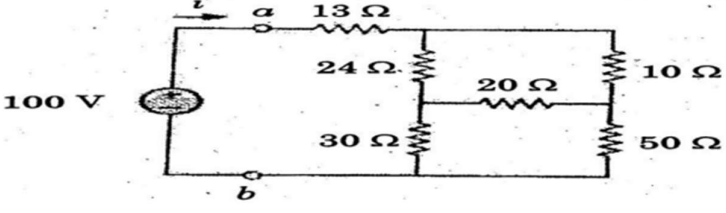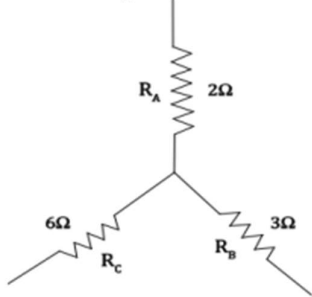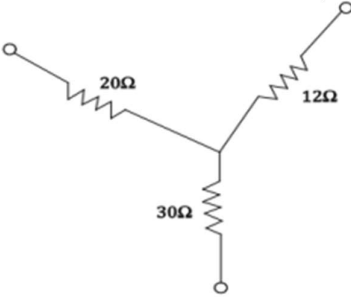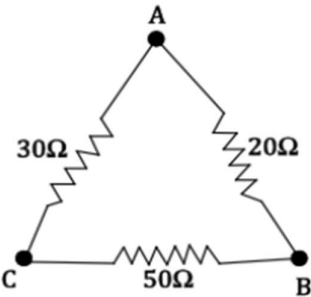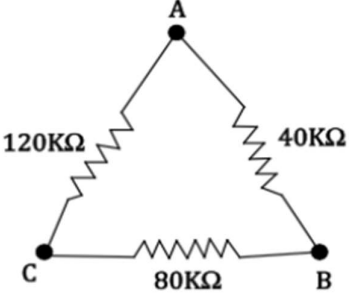			
12.	<p>Analyze the value of <math>R_L</math> for maximum power transfer and determine maximum power for the circuit given. (13)</p> 	BTL 6	Create
13.	<p>Obtain the equivalent resistance <math>R_{ab}</math> of the circuit given in Fig. and calculate the total current <math>i</math>. (13)</p> 	BTL 4	Analyze
14.	<p>(i) Analyze the following Star network into Delta network as shown in Fig. (06)</p>   <p>(ii) Analyze the following network Delta into Star network and find the value as shown in Fig. (07)</p>  	BTL 5	Evaluate
<b>PART-C</b>			
1.	<p>(a) Fig.1 shows a two D.C source network, the branch Current <math>I_1</math> and <math>I_2</math> are marked in it. By using Kirchoff's law,</p>	BTL 5	Evaluate

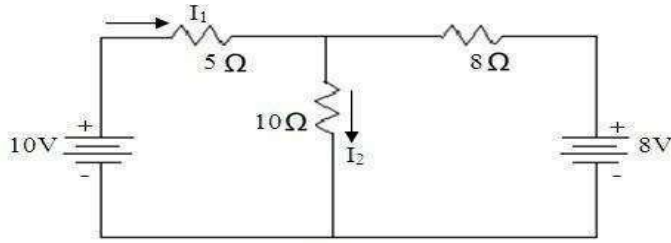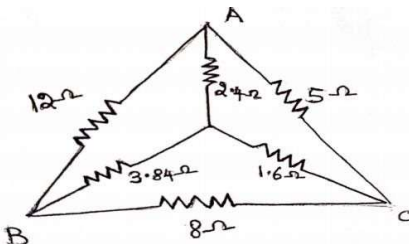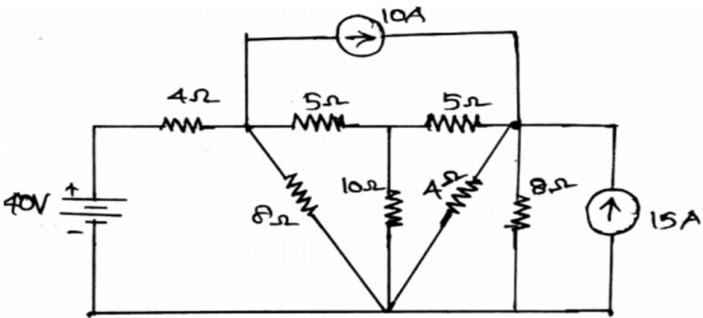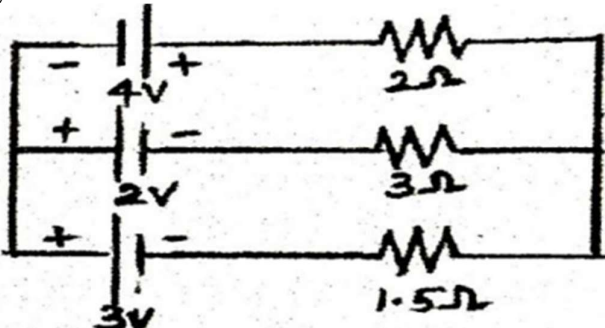	<p>calculate and examine the current <math>I_1</math>. (08)</p>  <p>Fig.1</p> <p>(b) A series circuit has <math>R=10\Omega</math>, <math>L=50\text{mH}</math> and <math>C=100\mu\text{F}</math> and is supplied and is applied with 200V, 50 Hz. Find and examine the value of: (1) Impedance (2) Current (3) Power (4) Power factor (5) Phase angle (6) Voltage drop across each element. (07)</p>	BTL 5	Evaluate
2.	<p>Evaluate the equivalent resistance of the circuit using star – delta conversion. (15)</p> 	BTL 6	Create
3.	<p>Use Nodal Voltage method and estimate the power dissipated in the 10 Ω resistance on the circuit shown in the Fig. (15)</p> 	BTL 5	Evaluate
4.	<p>(i) Determine the magnitude and direction of the current in the 2 V battery in the circuit. (07)</p>  <p>(ii) Determine the power dissipation in the 4Ω resistor of the given circuit shown in Fig. (08)</p>	BTL 6	Create

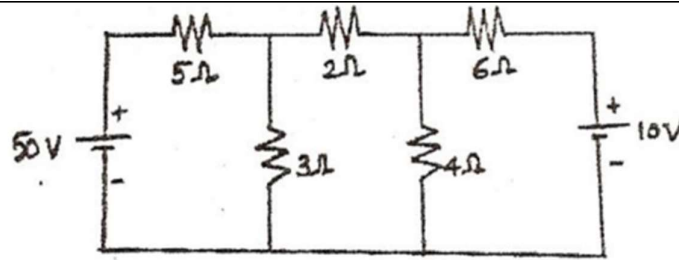

**UNIT II - ELECTRICAL MACHINES**

DC Machines: D.C generators & D.C motors: Principle of operation, constructions, types, Applications -A.C Machines: Types-Introduction to Alternators-Single Phase and Three phase induction motors: principle of operation, Types and Applications-Transformers: Principles of operation, Constructional Details, Types and Applications.

**PART – A**

S.No	Questions	BT Level	Competence
1.	What is the basic principle of operation of a dc motor?	BTL 1	Remember
2.	State Fleming’s left-hand rule.	BTL 1	Remember
3.	Distinguish motor action from generator action in a DC machine	BTL 2	Understand
4.	Differentiate critical speed and critical resistance of a DC generator.	BTL 4	Analyze
5.	Why DC shunt motor is called as constant speed drive?	BTL 1	Remember
6.	How does an alternator work?	BTL 1	Remember
7.	State the purpose of the following (i) Commutator (ii) Brushes in DC machine.	BTL 1	Remember
8.	In DC Generator, 8 poles, lap wound armature rotated at 350rpm to generate 260V, the useful flux/pole is 0.05Wb. If the armature has 120 slots. Calculate the number of conductors per slot.	BTL 3	Apply
9.	Why DC series motor should not be started without load?	BTL 2	Understand
10.	Point out two applications of Following DC motors (i) DC shunt motor (ii) DC series motor	BTL 1	Remember
11.	Define lenz Law.	BTL 2	Understand
12.	Express the term slip in Induction motor.	BTL 2	Understand
13.	With suitable formula, explain the following terms (i)Turn ratio of transformer. (ii) voltage regulation Of Transformer.	BTL 4	Analyze
14.	Illustrate why single-phase Induction motor is not self-starting.	BTL 4	Analyze
15.	Discuss the terms (i) Efficiency (ii) All day efficiency of single-phase transformer.	BTL 6	Create
16.	Plot the torque Slip Characteristics of Induction motor.	BTL 3	Apply
17.	Explain the working Principle of Transformer in Short.	BTL 6	Create
18.	Sketch the diagram of (i) core type and (ii) shell type transformer.	BTL 5	Evaluate
19.	Formulate the emf equation for Transformer.	BTL 3	Apply

20.	In a single-phase transformer, $N_p = 350$ turns, $N_s = 1050$ turns, $E_p = 400V$ . Calculate the value of secondary voltage ( $E_s$ ).	BTL 5	Evaluate
<b>PART-B</b>			
1.	Explain the construction, working of DC Generator and also explain the different parts. <b>(13)</b>	BTL 4	Analyze
2.	With a neat diagram explain the construction and working of D.C. Motor. List out the types of DC motor. <b>(13)</b>	BTL 1	Remember
3.	(i) Obtain the mathematical expression for generated EMF or EMF Equation of Generator and explain each term. <b>(05)</b> (ii) Calculate the generated EMF by 4-pole wave wound generator having 65 slots with 12 conductors per slot when driven at 1200 rpm the flux per pole is 0.02 Weber. <b>(08)</b>	BTL 4	Analyze
4.	With the help of schematic diagram Explain the principle of operation of Single-Phase induction motor and also explain why it is not a self-starting one. <b>(13)</b>	BTL 5	Evaluate
5.	Infer the terms such as (i) Faraday's Law of Electro Magnetic Induction <b>(3)</b> (ii) Fleming's Left- Hand rule. <b>(3)</b> (iii) Back or Counter emf. <b>(2)</b> (iv) Voltage Equation of DC Shunt Motor. <b>(2)</b> (v) Armature Torque of DC Motor. <b>(3)</b>	BTL 4	Analyze
6.	Explain in detail about the construction and working of three phase Induction motor. <b>(13)</b>	BTL 1	Remember
7.	(i) A 200V Dc shunt motor takes a total current of 100A and runs at 750 rpm. The resistance of the armature winding and of shunt field winding is $0.1 \Omega$ and $40\Omega$ respectively. Find the torque developed by the armature. <b>(07)</b> (ii) Derive the torque equation of DC motor. <b>(06)</b>	BTL 3 BTL 3	Apply Apply
8.	A 25kW, 250V, dc shunt generator has armature and field resistances of 0.06 ohm and 100 ohm respectively. Determine the total armature power developed when working (i) as a generator delivering 25 kW output and (ii) as a motor taking 25kW. <b>(13)</b>	BTL 3	Apply
9.	(i) Draw the circuit diagram for Single Phase Transformer <b>(06)</b> (ii) Explain the Principle, Construction, Working of it. <b>(07)</b>	BTL 4	Analyze
10.	(i) Derive the EMF Equation of Transformer. <b>(07)</b> (ii) A single phase 2000/250 V, 50Hz transformer has the core area of $36 \text{ cm}^2$ and maximum flux density of $6 \text{ Wb/m}^2$ . Calculate the number of turns on primary and secondary winding. <b>(06)</b>	BTL 6 BTL 3	Create Apply
11.	Describe the following terms in single phase transformer (i) Efficiency (ii) All day efficiency (iii) Losses in transformer (iv) Regulation of Transformer <b>(13)</b>	BTL 1	Remember
12.	(i) Distinguish core type and shell type transformers. <b>(06)</b> (ii) In core type transformer, the no load voltage is 5000/250 V, supply frequency 50Hz. Calculate the number of turns in each winding and the flux is about 0.06 Weber. <b>(07)</b>	BTL 2	Understand
13.	(i) Why the single-phase Induction motors are not Self-	BTL 2	Understand



	starting? (06) (ii) Compare and contrast the Squirrel cage and Slip ring Induction Motors. (07)	BTL 2	Understand
14.	Describe the following types of Single-Phase Induction Motor (i) Split phase Induction Motor (ii) Capacitor start type Induction Motor. (iii) Capacitor start Capacitor run Induction motor. (13)	BTL 2	Understand

**PART-C**

1.	Explain why 3-phase induction motor is self-starting and 1-phase is not. (15)	BTL 5	Evaluate
2.	A 30 KW, 220 V DC shunt machine has an armature resistance of 0.06 $\Omega$ and field resistance of 100 $\Omega$ . Calculate the total armature power developed when working as a motor taking 30 KW input. Also calculate the total armature power developed when working as a generator while delivering output of 30 KW. (15)	BTL 6	Create
3.	Sketch the speed-torque characteristic of a shunt motor at fixed field current. Explain the characteristic through relevant fundamental relationships of the machine. (15)	BTL 5	Evaluate
4.	The maximum flux density in the core of a 250 /3000-volt, 50 HZ single phase transformer is 1.2 wb/m <sup>2</sup> . If the emf per turn is 8 volts, determine: Primary and Secondary turns and Area of the core. (15)	BTL6	Create

**UNIT III - BASIC ELECTRICAL INSTRUMENTATION**

Introduction, classification of instruments, operating principles, essential features of measuring instruments (elementary Treatment only)- Moving coil, permanent magnet (PMMC) instruments, Moving Iron of Ammeters and Voltmeters Energy meter, Current Transformer, Potential Transformer.

**PART-A**

S.No	Questions	BT Level	Competence
1.	Classify measuring Instruments.	BTL 4	Analyze
2.	Name the basic elements used in measuring instrument?	BTL 2	Understand
3.	Point out the types of error occurs in measurement system?	BTL 4	Analyze
4.	Define the term calibration.	BTL 3	Apply
5.	Interpret the terms precision and sensitivity?	BTL 3	Apply
6.	Justify MI is used on both A.C and D.C.	BTL 6	Create
7.	Define static error.	BTL 3	Apply
8.	Draw the block diagram indicating functional elements of measurement system.	BTL 4	Analyze
9.	Compare limiting errors and instrumental errors.	BTL 1	Remember
10.	Name the torque which is absent in energy meter?	BTL 3	Apply
11.	How can we get true values from measurements?	BTL 1	Remember
12.	Why is the controlling torque needed in a measuring instrument?	BTL 1	Remember
13.	Name the types of torques required for the operation of	BTL 6	Create

	measuring instruments?		
14.	List the different types of possible errors in measurements.	BTL 6	Create
15.	Define the term creeping of an energy meter?	BTL 1	Remember
16.	Compare polarised and non-polarised instrument?	BTL 2	Understand
17.	Name which instrument can be used on ac only?	BTL 2	Understand
18.	Outline the advantages of PMMC instrument.	BTL 1	Remember
19.	What is meant by phantom loading?	BTL 5	Evaluate
20.	A 50 A, 230 V meter on full load test makes 61 revolutions in 37 sec. If the normal disc speed is 520 revolutions per kwhr. What is the percentage error?	BTL 5	Evaluate
<b>PART-B</b>			
1.	(i) Outline the block diagram showing the basic functional elements of an instrument and explain the functions of each. <b>(06)</b> (ii) Explain in detail about damping torque, controlling torque and deflecting torque. <b>(07)</b>	BTL 1	Remember
2.	(i) Define limiting errors. Derive the expression for relative limiting errors. <b>(05)</b> (ii) Describe the working of repulsion type moving iron instrument. <b>(08)</b>	BTL 1	Remember
3.	Draw and explain the static and dynamic characteristics of a measurement system. <b>(13)</b>	BTL 4	Analyze
4.	(i) Discuss the construction and working of PMMC instrument. <b>(07)</b> (ii) Derive the equation for deflection if the instruments are spring controlled. <b>(06)</b>	BTL 4	Analyze
5.	Describe in detail the different types of dynamic errors in a measurement system. <b>(13)</b>	BTL 4	Analyze
6.	Briefly explain the working of moving iron instruments. Mention its advantages and disadvantages. <b>(13)</b>	BTL 3	Apply
7.	Give the construction and principle of operation of single-phase induction type energy meter. <b>(13)</b>	BTL 2	Understand
8.	Describe in detail about the working principle of attraction-type moving iron instruments. <b>(13)</b>	BTL 3	Apply
9.	Distinguish between an attraction-type and a repulsion-type moving-iron instrument. <b>(13)</b>	BTL 2	Understand
10.	Discuss about the constructional details and working principle of a repulsion-type moving-iron instrument. <b>(13)</b>	BTL 5	Evaluate
11.	(i) Justify moving coil instrument can be used on DC only and not on AC circuits. <b>(05)</b> (ii) Derive the torque equations in PMMC instrument. <b>(08)</b>	BTL 2	Understand
12.	(i) Write briefly with neat figures on Principle of operation of a current transformer. <b>(06)</b> (ii) List out the essential features of measuring instruments <b>(07)</b>	BTL 6	Create
13.	(i) Explain the working of potential transformer and mention its applications. <b>(06)</b> (ii) Explain the working of single-phase energy meter. <b>(07)</b>	BTL 1	Remember
14.	Differentiate between a PMMC and dynamometer type		

	moving coil instrument. (13)	BTL 1	Remember
<b>PART-C</b>			
1.	Derive the expressions for shunt resistance and multiplier resistance. (15)	BTL 5	Evaluate
2.	Two ammeters are joined in series in a circuit carrying 10A. Ammeter has a resistance of 1000 $\Omega$ and is shunted by 0.02 $\Omega$ . The corresponding values for ammeter B are 1500 $\Omega$ and 0.01 $\Omega$ . What will the instruments read if the shunts are interchanged? (15)	BTL 6	Create
3.	Develop expressions for deflecting torque and control torque for a PMMC instrument and show that the scale of the instrument is linear. (15)	BTL 5	Evaluate
4.	Briefly Explain the construction and principle of operation of a 3-phase energy meter. (15)	BTL 6	Create
<b><u>UNIT IV -ELECTRICAL WIRING AND SAFETY</u></b>			
Cable and wire types and applications, Service mains, meter board and distribution board. Brief discussion on concealed conduit wiring. Two-way and three-way control. Elementary discussion on Circuit protective devices: fuse and Miniature Circuit Breaker (MCBs). Electric shock, precautions against shock, Objectives for Neutral and Earthing, types of earthing; pipe and plate earthing, Residual current circuit breaker.			
<b>PART-A</b>			
<b>S.No</b>	<b>Questions</b>	<b>BT Level</b>	<b>Competence</b>
1.	Point out the deciding factors of selection of wires.	BTL 4	Analyze
2.	Mention the basic requirements of fuses?	BTL 2	Understand
3.	State the importance of earthing.	BTL 1	Remember
4.	Classify domestic wiring	BTL 1	Remember
5.	Name the protective devices used in power systems?	BTL 1	Remember
6.	Sketch the wiring diagram of a tube light circuit.	BTL 1	Remember
7.	List out the various types of electrical wiring.	BTL 2	Understand
8.	What is the necessity of earthing?	BTL 2	Understand
9.	List out the different types of cables used for domestic wiring.	BTL 2	Understand
10.	Mention the purpose of neutral wire in an electrical distribution system.	BTL 2	Understand
11.	Classify distribution system.	BTL 3	Apply
12.	What is meant by feeder?	BTL 3	Apply
13.	Summarize the importance of fuse.	BTL 3	Apply
14.	Draw the circuit diagram of two-way switch controlling a single lamp.	BTL 2	Understand
15.	Give some advantages of plate earthing.	BTL 1	Remember
16.	Draw the symbol of circuit breaker.	BTL 4	Analyze
17.	Compare circuit breaker and fuse.	BTL 5	Evaluate
18.	Label the function of earth wire in an electrical distribution system.	BTL 5	Evaluate

19.	Expand the term ELCB.	BTL 6	Create
20.	List out the Safety precautions to be followed against electric shock?	BTL 6	Create
<b>PART-B</b>			
1.	(i) Briefly explain the types of wiring with neat diagram. (07) (ii) What is earthing? And write the necessity of earthing. (06)	BTL 1 BTL 1	Remember Remember
2.	With neat circuit diagram explain how to control a group of lamps from several places. (13)	BTL 1	Remember
3.	Sketch the circuit diagram of fluorescent lamp and explain the function of each component. (13)	BTL 1	Remember
4.	Briefly discuss about the construction, working and applications of HRC fuse. (13)	BTL 1	Remember
5.	Draw the schematic diagram of stair case lighting, i.e., one lamp controlled from two positions. Also draw the wiring diagram. (13)	BTL 2	Understand
6.	Discuss about the pipe earthing and plate earthing and also mention its importance. (13)	BTL 2	Understand
7.	Explain the construction and working of Energy meter with neat diagram. (13)	BTL 2	Understand
8.	Sketch the circuit diagram of tube light and explain the function of each component. (13)	BTL 3	Apply
9.	(i) List out the protective devices used in electrical power system and write its specifications and functions. (07) (ii) Express the formula for fuse rating with example. (06)	BTL 3	Apply
10.	(i) Examine the operation of two-way switch. (06) (ii) Describe in detail about the operation of three-way switch control. (07)	BTL 4	Analyze
11.	Explain in detail about the construction and working of Miniature circuit breaker. (13)	BTL 4	Analyze
12.	(i) Describe in detail about concealed conduit wiring. (07) (ii) Compare earthing and neutral. (06)	BTL 4 BTL 4	Analyze Analyze
13.	Discuss in detail on residual current circuit breaker. (13)	BTL 5	Evaluate
14.	(i) Enumerate Some of the safety measures to avoid electric shock. (07) (ii) Discuss about concealed conduit wiring. (06)	BTL 6 BTL 6	Create Create
<b>PART-C</b>			
1.	Sketch the circuit for a staircase lamp controlled from two positions. It should be possible to switch-on or switch-off the lamp by any of the two switches, one located upstairs and the other located downstairs. (15)	BTL 5	Evaluate
2.	Discuss the functions of grounding system in distribution networks. What are the effects of bad grounding on personnel working on power system networks? (15)	BTL 5	Evaluate
3.	Two lamps and one fan are to be controlled by independent switches placed on a single switch board. Draw the schematic circuit diagram. (15)	BTL 6	Create
4.	Draw a neat diagram of distribution board for domestic wiring and explain the function of each component used. (15)	BTL 6	Create

<b>UNIT V ELECTRICAL POWER SYSTEM AND ITS APPLICATION</b>			
Introduction to Power generation, distribution and Transmission. Power supply circuits with SMPS, UPS, Batteries, Power Tariffs, EMI and EMC.			
<b>PART-A</b>			
<b>S.No</b>	<b>Questions</b>	<b>BT Level</b>	<b>Competence</b>
1.	Examine the major equipment of a substation.	BTL 4	Analyze
2.	Name the three major components of electric power system.	BTL 5	Evaluate
3.	What is meant by primary transmission?	BTL 1	Remember
4.	Compare feeder and distributor.	BTL 1	Remember
5.	Classify distribution system based on the connections.	BTL 2	Understand
6.	How to reduce the power losses during transmission?	BTL 2	Understand
7.	Define the term Temperature coefficient of resistance.	BTL 6	Create
8.	Mention the methods to improve power factor in power system.	BTL 3	Apply
9.	Write any two examples for conventional sources and non-conventional sources.	BTL 1	Remember
10.	Define the term transmission efficiency.	BTL 1	Remember
11.	Sketch the single line diagram.	BTL 3	Apply
12.	Give few points on the advantages of HVDC system.	BTL 4	Analyze
13.	List out the function of SMPS.	BTL 2	Understand
14.	Expand the term UPS.	BTL 6	Create
15.	Compare online and offline UPS.	BTL 1	Remember
16.	Define the term power tariff.	BTL 4	Analyze
17.	Write few about tariff calculation on domestic applications.	BTL 5	Evaluate
18.	How battery is rated?	BTL 3	Apply
19.	Expand the terms EMI and EMC.	BTL 2	Understand
20.	Point out the effects of EMI?	BTL 1	Remember
<b>PART-B</b>			
1.	(i) Compare ring main distribution system and the radial system. <b>(06)</b> (ii) Discuss various types of supply in power system. <b>(07)</b>	BTL 6	Create
2.	(i) Draw single line diagram of a power system. <b>(07)</b> (ii) List out the major components used in power system and also explain its working. <b>(06)</b>	BTL 3	Apply
3.	Differentiate 3-phase 4-wire system with the single-phase system. <b>(13)</b>	BTL 4	Analyze
4.	(i) Describe the function of Switch mode power supply. Mention its applications. <b>(07)</b> (ii) Briefly discuss various supply in power system. <b>(06)</b>	BTL 3	Apply
5.	(i) Analyze the causes of low p.f. in power system. <b>(06)</b> (ii) Discuss various methods of improving the power factor. <b>(07)</b>	BTL 4	Analyze
6.	Briefly discuss various non-conventional methods of generating electrical energy. <b>(13)</b>	BTL 2	Understand
7.	(i) Why skin effect occurs in transmission line? and what are the	BTL 4	Analyze

	factors affecting it? (ii) Interpret the factors to be considered for site selection of power plant. <b>(13)</b>	BTL 4	Analyze
8.	With neat diagram explain the function of UPS with its components. <b>(13)</b>	BTL 1	Remember
9.	What is SMPS? Bring out the components used in SMPS and also mention its advantages and disadvantages. <b>(13)</b>	BTL 2	Understand
10.	(i) Classify the battery and also mention its advantage and disadvantages. <b>(05)</b> (ii) Draw the block diagram of online UPS and offline UPS. <b>(08)</b>	BTL 1 BTL 1	Remember Remember
11.	(i) Summarize the concept Power Tariff used for energy consumption. <b>(07)</b> (ii) Tabulate the classification of Power Tariff. <b>(06)</b>	BTL5	Evaluate
12.	Briefly discuss on the properties and types of Insulating material. Also mention the advantage and disadvantages of each type. <b>(13)</b>	BTL 1	Remember
13.	Discriminate few points about HVDC system. <b>(13)</b>	BTL 2	Understand
14.	(i) Define the term EMI and EMC <b>(04)</b> (ii) Explain in detail about the causes, effects and controlling techniques of EMI. <b>(09)</b>	BTL 1	Remember
<b>PART-C</b>			
1.	Discuss the performance of static capacitor with a synchronous condenser as a power factor improvement device. <b>(15)</b>	BTL 5	Evaluate
2.	In DC two-wire system, a feeder is working on 250 V to supply a constant load. If the supply voltage is increased to 480 V with power transmitted remaining the same, compute the percentage saving in conductor material. <b>(15)</b>	BTL 5	Evaluate
3.	Describe the concept Power Tariff used for energy consumption and also list out its types. <b>(15)</b>	BTL 6	Create
4.	Explain in detail about the various methods of improving the power factor and also point out the causes that producing it <b>(15)</b>	BTL 6	Create