

SRM VALLIAMMAI ENGINEERING COLLEGE

SRM Nagar, Kattankulathur – 603 203

**DEPARTMENT OF
ELECTRICAL AND ELECTRONICS ENGINEERING
B.E
QUESTION BANK**



VI SEMESTER

1905606 – MODERN POWER CONVERTERS

Regulation – 2019

Academic Year 2021-22(EVEN)

Prepared by

**Ms. A. Dhivya,
Assistant Professor (O.G) / EEE**



SRM VALLIAMMAI ENGINEERING COLLEGE

SRM Nagar, Kattankulathur – 603 203.

DEPARTMENT OF EEE



QUESTION BANK

SUBJECT : 1905606 – Modern Power Converters

SEM / YEAR: VI / 2021-22 (Even)

UNIT I SWITCHED MODE POWER SUPPLIES (SMPS)				
DC Power supplies and Classification; Switched mode dc power supplies - with and without isolation, single and multiple outputs; Closed loop control and regulation; Design examples on converter and closed loop performance.				
PART – A				
Q.No	Questions	BTL Level	Domain	COs
1.	What is meant by SMPS?	BTL-2	Understand	CO1
2.	What are the types of SMPS?	BTL-1	Remember	CO1
3.	List the Advantages of SMPS.	BTL-1	Remember	CO1
4.	List the Disadvantages of SMPS.	BTL-6	Create	CO1
5.	List out the difference between fly back and push pull topologies.	BTL-5	Evaluate	CO1
6.	Obtain the input-output voltage and current relation as a function of duty ratio for a Buck-Boost dc-dc converter in continuous conduction mode.	BTL-3	Apply	CO1
7.	What is a switching mode regulator?	BTL-1	Remember	CO1
8.	How Dc Power supplies are classified?	BTL-6	Create	CO1
9.	List the types of isolated SMPS	BTL-2	Understand	CO1
10.	List the types of non-isolated SMPS	BTL-2	Understand	CO1
11.	What are the necessary requirements for a power supply to be used in Industrial applications?	BTL-1	Remember	CO1
12.	What are the performance parameters of a converter?	BTL-5	Evaluate	CO1
13.	What is multioutput boost converter?	BTL-1	Remember	CO1
14.	Which type of isolated converters will be used for low voltage and high voltage applications?	BTL-2	Understand	CO1
15.	Draw the block diagram of closed loop control of converters.	BTL-4	Analyse	CO1
16.	What are the four basic types of switching mode regulators.?	BTL-3	Apply	CO1
17.	Write the expression for the output voltage of half bridge converter.	BTL-3	Apply	CO1
18.	Define duty cycle.	BTL-4	Analyse	CO1

19.	Write the expression for the output voltage of buck and boost converter.	BTL-4	Analyse	CO1
20.	With a help of block diagram explain the basic principle of operation of SMPS	BTL-1	Remember	CO1
PART – B				
1.	<ul style="list-style-type: none"> i. What is SMPS? Give its operating principle and industrial applications. (6) ii. List the various types of SMPSs. Describe SMPS with a pushpull configuration. (7) 	BTL-2	Understand	CO1
2.	Describe flyback SMPS with relevant equivalent circuits and waveforms. Derive the various. expressions for voltages and currents involved. (13)	BTL-2	Understand	CO1
3.	Describe SMPSs using half-bridge and full-bridge configurations. Enumerate the advantages and disadvantages possessed by SMPSs. (13)	BTL-1	Remember	CO1
4.	Discuss operation of Cuk converter. Derive the relation between duty ratio and input voltage. (13)	BTL-4	Analyse	CO1
5.	What is the difference between isolated and non-isolated dc power supply? Explain fly back converter topology with diagram and wave forms. (13)	BTL-1	Remember	CO1
6.	<ul style="list-style-type: none"> i. State important advantages, disadvantages and applications of SMPS. (3) ii. Discuss design criterion of SMPS. (4) iii. Discuss operation of Flyback converter. Draw its circuit diagram and waveforms. (6) 	BTL-2	Understand	CO1
7.	<ul style="list-style-type: none"> i. Explain fly back converter topology with diagram and waveforms (7) ii. Compare buck, boost and buck-boost converter with reference to technical parameters. (6) 	BTL-4	Analyse	CO1
8.	Illustrate the push pull converter with neat circuit diagram & waveform and derive the equation of output voltage in terms of input voltage & duty cycle. (13)	BTL-3	Apply	CO1
9.	<ul style="list-style-type: none"> i. Compare switching voltage regulator with linear voltage regulator. (3) ii. Explain half bridge converter. (4) iii. Discuss operation of Buck converter in continuous and discontinuous mode. (6) 	BTL-1	Remember	CO1
10.	<ul style="list-style-type: none"> i. Explain boost switching regulators. (3) ii. Explain fly back converter. (4) iii. Discuss operation of Push pull converter type switched mode dc power supply along with necessary waveforms. (6) 	BTL-1	Remember	CO1

11.	With neat circuit diagram & waveform explain the operation of a BOOST converter in CCM and Derive the equation of (1) Peak to Peak Inductor Current (2) Peak to Peak Capacitor Voltage (3) Critical value of inductor & Capacitor. (13)	BTL-6	Create	CO1
12.	Design and describe the analysis of buck boost converter. (13)	BTL-3	Apply	CO1
13.	Design a Buck-Boost converter circuit having parameters, input voltage =24 V, D=0.4, load resistance =5 ohm, L=20 micro H,C=80 micro F. Determine the output voltage, average inductor current, Maximum and minimum value of inductor current and the output voltage ripple. Assume a switching frequency of 100 kHz. (13)	BTL-5	Evaluate	CO1
14.	Draw the circuit diagram and explain the operation of a full bridge converter and draw the load current and load voltage waveform. (13)	BTL-4	Analyze	CO1
PART – C				
1	Design a Buck converter to produce an output voltage of 18 V across 10 ohm load resistance. The output voltage ripple must not exceed 0.5 percent. The DC supply is 48 V. Design for continuous inductor current. Find out the duty ratio, the values of inductance and capacitor. (15)	BTL-5	Evaluate	CO1
2	Draw the circuit diagram and explain the operation of a full bridge converter and draw the load current and load voltage waveform. (15)	BTL-6	Create	CO1
3	The buck-boost regulator has an input voltage = 12 V, duty cycle = 0.25, switching frequency = 25 kHz, inductor = 150 μ H, filter capacitor = 220 μ F and average load current = 1.25 A. Determine (a) Average output voltage (b) Peak to peak output voltage ripple (c) Peak to peak ripple current (d) Peak current of switch (e) Critical value of L and C. (15)	BTL-6	Create	CO1
4	A flyback SMPS supplies. a load of 40A at 5V. The source voltage is 240V dc and the transformer initial magnetizing current is 0.4 A. The power MOSFET is operating at a frequency of 50 kHz with a duty cycle of 0.4. Determine the transformer turns ratio from primary to secondary and its inductance. Assume ideal components and no ripple in load voltage. Find also the open-circuit voltage across the semiconductor device. (15)	BTL-5	Evaluate	CO1

UNIT II AC-DC CONVERTERS

Switched mode AC-DC converters. synchronous rectification - single and three phase topologies - switching techniques - high input power factor. reduced input current harmonic distortion. improved efficiency. with and without input-output isolation. performance indices design examples-PWM Rectifiers, Power factor improvement techniques

PART – A

Q.No	Questions	BTL Level	Domain	COs
1.	Define input power factor.	BTL-1	Remember	CO2
2.	List out the different types of controlled rectifier.	BTL-1	Remember	CO2
3.	Quote the expression for the RMS output voltage in single phase fully controlled rectifier with RLE load.	BTL-2	Understand	CO2
4.	Generalize the expression for the Average and RMS output voltage in single phase semi converter.	BTL-6	Create	CO2
5.	Evaluate the various applications of controlled converter.	BTL-5	Evaluate	CO2
6.	Examine the function of freewheeling diode in controlled rectifier.	BTL-3	Apply	CO2
7.	List the two configuration of single phase two pulse-controlled rectifier.	BTL-2	Understand	CO2
8.	Define Harmonic Distortion.	BTL-6	Create	CO2
9.	Draw the output current waveform of single phase semi controlled AC-DC converter fed RL load for $\alpha = 30^\circ$.	BTL-1	Remember	CO2
10.	Give the power balance equation in converter circuits.	BTL-2	Understand	CO2
11.	Define ripple and distortion factor.	BTL-1	Remember	CO2
12.	What do you mean by Synchronous Rectification?	BTL-5	Evaluate	CO2
13.	Define voltage ripple factor.	BTL-1	Remember	CO2
14.	Describe the advantages of using a freewheeling diode in a semi converter circuit.	BTL-4	Analyse	CO2
15.	Differentiate the rectifier mode and inverter mode in single phase converters.	BTL-2	Understand	CO2
16.	Illustrate the effect of source inductance in single phase converters.	BTL-3	Apply	CO2
17.	Examine the conditions required for operating the full converter in the inverter mode.	BTL-3	Apply	CO2
18.	Explain the reactive power.	BTL-4	Analyze	CO2
19.	Point out the power factor improvement techniques.	BTL-4	Analyze	CO2
20.	Distinguish between symmetric and asymmetric semiconductor configuration.	BTL-1	Remember	CO2

PART – B

1.	Discuss on a single-phase full converter feeding RLE load. (13)	BTL-2	Understand	CO2
----	---	-------	------------	-----

2.	Describe the principle of operation of a single-phase semi-converter with freewheeling diodes. Sketch the circuit diagram and draw the waveforms for source voltage, output voltage, thyristor currents, diode currents, source current, load current and freewheeling diode current assuming a large inductor in the load. Derive the expression for average output voltage and also derive the expression for RMS output voltage. (13)	BTL-2	Understand	CO2
3.	Examine the principle of operation for a single-phase full-converter with R-L load and no freewheeling diode. Sketch the circuit diagram and draw the waveforms for source voltage, output voltage, load current and source current assuming a large inductor and no ripple in the output current. Derive the expression for RMS output voltage. (13)	BTL-4	Remember	CO2
4.	Analyse the single-phase dual converter. (13)	BTL-4	Analyse	CO2
5.	Explain the Operation of Three Phase 3 Pulse Converter with R Load. Derive Average Output Voltage. (13)	BTL-1	Remember	CO2
6.	Discuss the operation of single phase fully controlled rectifier supplying RL load with neat Waveforms. Also derive the expression for the average output voltage?	BTL-2	Understand	CO2
7.	A 3-phase bridge converter is used for obtaining a regulated Dc output voltage. The supply voltage is 440V and the firing angle is maintained at 60° so that the load current is 15 A. Calculate (13) 1)DC output voltage 2)active and reactive power input 3)DC output voltage if freewheeling diode is connected	BTL-4	Analyse	CO2
8.	Examine on a three-phase operation full controlled bridge converter. (13)	BTL-3	Apply	CO2
9.	Describe the Three phase operation of semi-converter R and RL load. (13)	BTL-1	Remember	CO2
10.	A six-pulse thyristor converter connected on the secondary of delta /star connected 6.6 kV /415V ,50 Hz transformer is supplying to 460 V,200 A DC load. Identify the following (i) converter firing angle (ii)dc power delivered by the converter (iii)AC line current (iv)RMS value of the device current. (13)	BTL-2	Understand	CO2
11.	Generalize the Three phase operation of semi-converter RLE load. (13)	BTL-6	Create	CO2
12.	Demonstrate the power factor improvement techniques and explain the reactive power. (13)	BTL-3	Apply	CO2
13.	Evaluate the inverter mode of operation for thyristor converters. (13)	BTL-5	Evaluate	CO2

14.	With relevant waveforms, derive the expression for average and rms value of output voltage in a single phase full controlled converter with RL load. (13)	BTL-4	Analyze	CO2
PART – C				
1	The single-phase full converter has a RL load having $L=6.5 \text{ mH}$, $R= 0.5\Omega$ and $E=10\text{V}$.The input voltage is $V_s=120\text{V}$ at (rms)60 Hz. Evaluate the following (a)the load current I_{LO} at $\omega t=\alpha=60^\circ$, (b)the average thyristor current I_A , (c)the rms thyristor current I_R , (d)the rms output current I_{rms} , (e)the average output I_{dc} , and (f)the critical delay angle α_c . (15)	BTL-5	Evaluate	CO2
2	The single-phase dual converter is operated from a 120V, 60 Hz supply and the load resistance is $R=10\Omega$. The circulating inductance is $L_r=40\text{mH}$.delay angles are $\alpha_1=60^\circ$ and $\alpha_2=120^\circ$.Design the peak circulating current and peak current of converter1. (15)	BTL-6	Create	CO2
3	Integrate the single-phase full converter feeding RLE load and PWM rectifiers. (15)	BTL-6	Create	CO2
4	Summarize the Three phase operation of semi-converter R and RL load and evaluate the power factor improvement techniques and explain the reactive power. (15)	BTL-5	Evaluate	CO2

UNIT III DC-AC CONVERTERS

Multi-level Inversion - concept, classification of multilevel inverters, Principle of operation, main features and analysis of Diode clamped, Flying capacitor and cascaded multilevel inverters; Modulation schemes.

PART - A

Q.No	Questions	BTL Level	Domain	COs
1.	Why higher levels are not possible with diode clamped multilevel inverters?	BTL-2	Understand	CO3
2.	Mention the applications of multi-level inverter.	BTL-1	Remember	CO3
3.	How many switching device and clamping diodes are present in m-level diode clamped inverters?	BTL-1	Remember	CO3
4.	Draw the circuit diagram of five level flying capacitor of single-phase inverter?	BTL-6	Create	CO3
5.	What are the features of a multilevel inverter?	BTL-5	Evaluate	CO3
6.	Compare diode clamped with flying capacitors multilevel inverter.	BTL-3	Apply	CO3
7.	What are the advantages of multilevel inverter?	BTL-1	Remember	CO3
8.	What are the conditions needed for the structure of multilevel inverter?	BTL-6	Create	CO3
9.	Give the classification of multilevel inverter?	BTL-2	Understand	CO3
10.	What are the devices required for an m-level inverter in Diode-Clamped Multilevel inverter?	BTL-2	Understand	CO3
11.	What are the rules governing the switching of an m-level inverter?	BTL-1	Remember	CO3
12.	Give the Different type of Multi level inverters?	BTL-5	Evaluate	CO3
13.	How selective harmonics elimination is achieved in multilevel inverters?	BTL-1	Remember	CO3
14.	What is the main disadvantage of diode clamped multilevel inverters?	BTL-4	Analyze	CO3
15.	List the merits and demerits of cascaded H bridge multilevel inverters.	BTL-2	Understand	CO3
16.	What is a flying capacitor?	BTL-3	Apply	CO3
17.	What is the main feature of the cascaded multilevel inverter?	BTL-3	Apply	CO3
18.	What is the basic concept of multilevel inverter?	BTL-4	Analyze	CO3
19.	What are the disadvantages of diode clamped multilevel inverter?	BTL-4	Analyze	CO3
20.	What are features of diode-clamped inverter?	BTL-1	Remember	CO3

PART - B

1.	With circuit diagram and waveform explain the operation of five level flying capacitor multilevel inverter. (13)	BTL-2	Understand	CO3
----	--	-------	------------	-----

2.	Explain the principle of operation of a single phase multilevel cascaded H-bridge inverter with neat	BTL-2	Understand	CO3
3.	With a neat sketch explain the operation of diode clamped multilevel inverter. (13)	BTL-1	Remember	CO3
4.	<ul style="list-style-type: none"> i. Compare different multilevel inverters in terms of number of components per leg. (7) ii. Describe the applications of multilevel inverter for reactive power compensation. (6) 	BTL-4	Analyze	CO3
5.	Explain the five-level capacitor clamped multilevel inverter with necessary circuits and waveforms. (13)	BTL-1	Remember	CO3
6.	<ul style="list-style-type: none"> i. What is multilevel inverter? List different types of multilevel inverters and explain its principle of operation. (7) ii. Compare different multilevel inverters based on the requirement of number of power electronic devices. (6) 	BTL-2	Understand	CO3
7.	With a neat schematic diagram, explain the operation of a three-phase five level Cascaded Multilevel Inverter. Also list their merits. (13)	BTL-4	Analyze	CO3
8.	What is an asymmetric multilevel inverter? Explain how more output voltage is obtained with a smaller number of H bridge cells. (13)	BTL-3	Apply	CO3
9.	Draw and explain the diode clamped type MLI and discuss characteristics. (13)	BTL-1	Remember	CO3
10.	Draw and explain the Cascaded type MLI and discuss characteristics. (13)	BTL-1	Remember	CO3
11.	Explain the operation of FCML inverter in details. (13)	BTL-6	Create	CO3
12.	Draw and explain the Basic concept of multilevel inverter? (13)	BTL-3	Apply	CO3
13.	With neat diagram describe the operation of diode-clamped multilevel inverter. Also explain applications of multilevel inverter? (13)	BTL-5	Evaluate	CO3
14.	Explain the features, applications, advantages and disadvantages of multilevel inverter. (13)	BTL-4	Analyze	CO3
PART C				
1	Draw and explain the operation of a four-level diode clamped multilevel inverter. Write the inverter relationship for R phase. Derive the expression for transistor voltage, freewheeling diode current, capacitor junction current and clamping diode current. (15)	BTL-5	Evaluate	CO3
2	Compare and contrast the different configurations of multilevel inverters based on the various aspects involved in their design. (15)	BTL-6	Create	CO3
3	A single-phase diode clamped inverter has $m=5$. Find the peak voltage and current ratings of diodes and switching devices if $V_{dc}=5KV$ and $I_o=50\sin(\phi-\pi/3)$. (15)	BTL-6	Create	CO3

4	How are the MLI used for reactive power compensator and controlling the flow the power between two systems? Discuss. (15)	BTL-5	Evaluate	CO3
---	--	-------	----------	-----

UNIT IV AC-AC CONVERTERS WITH AND WITHOUT DC LINK

Matrix converters. Basic topology of matrix converter; Commutation – current path; Modulation techniques - scalar modulation, indirect modulation; Matrix converter as only AC-DC converter; AC-AC converter with DC link - topologies and operation - with and without resonance link - converter with dc link converter; Performance comparison with matrix converter with DC link converters.

PART - A

Q.No	Questions	BTL Level	Domain	COs
1.	What is a matrix converter?	BTL-2	Understand	CO4
2.	What are the advantages of using matrix converter?	BTL-1	Remember	CO4
3.	What are the disadvantages of matrix converter?	BTL-1	Remember	CO4
4.	Write the control methods of matrix converter.	BTL-6	Create	CO4
5.	Define Commutation.	BTL-5	Evaluate	CO4
6.	Draw the basic topology of matrix converter.	BTL-3	Apply	CO4
7.	Write the transfer matrix that represents the state of the converter matrix.	BTL-1	Remember	CO4
8.	Define Dead time commutation.	BTL-6	Create	CO4
9.	Define overlap commutation.	BTL-2	Understand	CO4
10.	What are the two ways to perform safe commutation?	BTL-2	Understand	CO4
11.	What are the steps to perform commutation in matrix converter?	BTL-1	Remember	CO4
12.	Define Scalar modulation.	BTL-5	Evaluate	CO4
13.	What is meant by indirect modulation?	BTL-1	Remember	CO4
14.	Draw the circuit diagram of AC-AC converter with DC link.	BTL-4	Analyse	CO4
15.	What is meant by resonant dc link converter?	BTL-2	Understand	CO4
16.	What are the advantage and disadvantage of DC link converter?	BTL-3	Apply	CO4
17.	Compare the performance of matrix converter with DC link converter.	BTL-3	Apply	CO4
18.	What are the types of resonant DC link converter?	BTL-4	Analyse	CO4
19.	Draw the circuit diagram of AC-AC converter without DC link.	BTL-4	Analyse	CO4
20.	Draw the circuit diagram of parallel resonant DC link converter.	BTL-1	Remember	CO4

PART - B

1.	Explain the basic topology of matrix converter. (13)	BTL-2	Understand	CO4
2.	With circuit Diagram, explain the current path using two step commutation strategy. (13)	BTL-2	Understand	CO4
3.	Explain the principle of operation of active and passive clamped resonant converters. (13)	BTL-1	Remember	CO4

4.	Explain in detail about the scalar and indirect modulation in matrix converter. (13)	BTL-4	Analyse	CO4
5.	Explain in detail about the topology and operation of AC-AC converter with resonant link. (13)	BTL-1	Remember	CO4
6.	Briefly explain the bidirectional switch commutation techniques. (13)	BTL-2	Understand	CO4
7.	With neat circuit diagram explain the topology and operation of AC-AC Converter with DC Link. (13)	BTL-4	Analyse	CO4
8.	With neat circuit diagram, explain the principle of operation parallel resonant DC link and Series resonant link DC converter. (13)	BTL-3	Apply	CO4
9.	Explain in detail about the topology and operation of AC-AC converter without resonant link. (13)	BTL-1	Remember	CO4
10.	Explain the current path in matrix converter with four step commutation strategy. (13)	BTL-1	Remember	CO4
11.	With neat circuit diagram, explain the principle of operation pole commutated DC link converter. (13)	BTL-6	Create	CO4
12.	Explain the modulation techniques for matrix converter. (13)	BTL-3	Apply	CO4
13.	With neat circuit diagram explain the topology and operation of AC-AC Converter without DC Link.	BTL-5	Evaluate	CO4
14.	Compare the operation of Matrix converter with DC Link Converter. (13)	BTL-4	Analyse	CO4
PART C				
1	A single-phase full wave ac voltage controller has a resistive load of 5Ω and an input voltage 230 V, 50 Hz. The firing angle of thyristors T_1 and T_2 is 120 degrees. Evaluate the (i) the RMS value of load voltage (ii)input power factor, (iii)average value of current of thyristor (iv)RMS current of thyristor (v)load power. (15)	BTL-5	Evaluate	CO4
2	Examine the operation of a 3phase AC voltage regulator having six thyristors with neat sketches of voltage waveforms. (15)	BTL-6	Create	CO4
3	Explain the basic topology and operation of matrix converter with its modulation strategies. (15)	BTL-6	Create	CO4
4	i. Compare the Cyclo converter and DC link converter. (8) ii. Explain the matrix converter. (7)	BTL-5	Evaluate	CO4

UNIT V SOFT-SWITCHING POWER CONVERTERS

Soft switching techniques. ZVS, ZCS, quasi resonance operation; Performance comparison hard switched and soft switched converters.AC-DC converter, DC-DC converter, DC-AC converter.; Resonant DC power supplies.

PART - A

Q.No	Questio	BTL Level	Domain	COs
1.	What are the advantages of ZCS resonant converter?	BTL-2	Understand	CO5
2.	What is the principal of zero-voltage switching resonant converters?	BTL-1	Remember	CO5
3.	What is the principal of zero-current switching resonant converters?	BTL-1	Remember	CO5
4.	What are advantages of ZVS resonant converter?	BTL-6	Create	CO5
5.	Draw the circuit diagram of resonant dc-link inverter.	BTL-5	Evaluate	CO5
6.	Compare ZVS and ZCS?	BTL-3	Apply	CO5
7.	What is resonant DC-link inverter?	BTL-1	Remember	CO5
8.	Define ZVS resonant converter?	BTL-6	Create	CO5
9.	Define ZCS resonant Converter?	BTL-2	Understand	CO5
10.	What are resonant converters? List their merits over switched converters.	BTL-2	Understand	CO5
11.	Write the various categories of resonant converters.	BTL-1	Remember	CO5
12.	What is a quasi-resonant converter?	BTL-5	Evaluate	CO5
13.	Differentiate briefly between quasi resonant and resonant converter.	BTL-1	Remember	CO5
14.	What do you mean by resonant switch? List the favourable features over PWN Switches.	BTL-4	Analyse	CO5
15.	Describe the switching loss.	BTL-2	Understand	CO5
16.	Define the hard switching.	BTL-3	Apply	CO5
17.	Quote the basic principle of soft switching.	BTL-3	Apply	CO5
18.	What are the advantages of soft switching over hard switching?	BTL-4	Analyse	CO5
19.	Compare the hard switching and soft switching.	BTL-4	Analyse	CO5
20.	How is the output voltage controlled in a series resonant inverter?	BTL-1	Remember	CO5

PART - B

1.	Draw and explain the zero-current switching resonant converters? (13)	BTL-2	Understand	CO5
2.	Draw and explain the zero-voltage switching resonant converters? (13)	BTL-2	Understand	CO5
3.	Summarize the basic principles of soft switching and hard switching. (13)	BTL-1	Remember	CO5

4.	Compare the Zero Current Switching (ZCS)/ Zero Voltage Switching (ZVS). (13)	BTL-4	Analyse	CO5
5.	Draw and explain the various types of zero current and zero voltage switch topology. (13)	BTL-1	Remember	CO5
6.	Draw and explain briefly the operation of resonant dc link inverter. (13)	BTL-2	Understand	CO5
7.	With neat circuit diagram explain the principle of operation and working of Resonant DC Power supplies. (13)	BTL-4	Analyse	CO5
8.	Summarize the performance comparison of hard switched and soft switched converters. (13)	BTL-3	Apply	CO5
9.	With a help of neat circuit diagram and associated waveforms explain the operation of half wave and full wave mode of ZCS Resonant buck converters. (13)	BTL-1	Remember	CO5
10.	With a help of neat circuit diagram and associated waveforms explain the operation of half wave and full wave mode of ZVS Resonant buck converters. (13)	BTL-1	Remember	CO5
11.	With a help of neat circuit diagram and waveforms explain the operation of class E resonant rectifiers. (13)	BTL-6	Create	CO5
12.	Describe the operation of resonant DC link inverters with zero voltage switching. Draw necessary circuits and waveforms. (13)	BTL-3	Apply	CO5
13.	Draw and explain the operation of ZVS Forward and flyback converter. (13)	BTL-5	Evaluate	CO5
14.	Draw and explain the operation of ZVS half bridge and ZVS full bridge PWM converter. (13)	BTL-4	Analyse	CO5
PART - C				
1	Summarize the series loaded resonant converter and parallel loaded resonant converter. (15)	BTL-5	Evaluate	CO5
2	Evaluate the Buck-Boost ZCS Quasi Resonant DC-DC Converter. (15)	BTL-6	Create	CO5
3	ZVS buck converter operates in half wave mode with $E_{dc} = 35$ V, $E_o = 24$ V, $f_r = 500$ KHz and $P_o = 24$ Determine the following (15) i. Values of resonant components L_r and C_r ii. Peak voltage rating of the resonant capacitor iii. Charging and discharging period of capacitor.	BTL-6	Create	CO5
4	ZCS resonant converter operates with $E_{dc} = 18$ V, $E_o = 12$ V, $f_r = 1$ MHz and $P_o = 12$ W. Determine the following: (15) i. Values of resonant components L_r and C_r ii. peak switch current iii. peak voltage rating of the resonant capacitor C_r .	BTL-5	Evaluate	CO5

COURSE OUTCOME:

1. Ability to suggest converters for AC-DC conversion and SMPS.
2. Ability to study about the concepts of AC – DC converters.
3. Ability to study about the concepts of DC – AC converters.
4. Ability to understand basics of AC-AC converters with and without DC link.
5. Learners will attain knowledge about soft switching power converter.