

# SRM VALLIAMMAI ENGINEERING COLLEGE

*(An Autonomous Institution)*

SRM Nagar, Kattankulathur – 603 203.

## QUESTION BANK



### III SEMESTER

**EE3363 Electric Circuit Analysis  
(Common to EEE, ECE, EIE & MDE)**

**Regulation – 2023  
Academic Year 2025–2026 (ODD SEM)**

*Prepared by*

**Dr. M. Banu Sundareswari , AP/EIE**

**Dr. K. Durgadevi, AP/ECE**

**Dr. J. Ganesan, AP / MDE**

**Ms.S.Abirami, AP/ECE**

**Mr. V. Prasanan, AP/ECE**

**Ms.R.Elavarasi, AP/EEE**



# SRM VALLIAMMAI ENGINEERING COLLEGE

(An Autonomous Institution)  
SRM Nagar, Kattankulathur – 603 203.







## DEPARTMENT OF ELECTRONICS AND INSTRUMENTATION ENGINEERING QUESTION BANK






### UNIT I - BASIC CIRCUITS ANALYSIS

**Ohm's Law -Kirchhoff 's Laws – DC Circuits – Resistors in series and parallel circuits - A.C Circuits – Average and RMS Value –Complex Impedance – Phasor diagram - Real and Reactive Power, Power Factor, Energy -Mesh current and node voltage methods of analysis D.C and A.C Circuits**

#### PART – A

Q.No	Questions	CO	BT Level	Competence
1.	What are active elements and passive elements?	CO1	BTL1	Remember
2.	State Ohm's Law.	CO1	BTL1	Remember
3.	Mention the limitations of Ohm's Law.	CO1	BTL1	Remember
4.	Write Kirchoff's Law mathematically.	CO1	BTL1	Remember
5.	State two salient points for a series combination of resistors.	CO1	BTL1	Remember
6.	State two salient points for parallel combination of resistors.	CO1	BTL1	Remember
7.	Write the Kirchoff's Voltage Law	CO1	BTL2	Understand
8.	Draw the symbolic representation of the Voltage Source and current Source	CO1	BTL2	Understand
9.	Write the expression for Form factor	CO1	BTL2	Understand
10.	Define Power factor.	CO1	BTL2	Understand
11.	Give the relationship between apparent power, average power & reactive power.	CO1	BTL2	Understand
12.	If two resistors of equal resistance R is connected in series, then what is the equivalent resistance?	CO1	BTL3	Apply
13.	If two resistors of equal resistance R is connected in parallel, then what is the equivalent resistance?	CO1	BTL3	Apply
14.	Two resistors 4 $\Omega$ and 6 $\Omega$ are connected in parallel. The total current flowing through the resistors is 5A. Find the current flowing through each resistor.	CO1	BTL3	Apply
15.	Two capacitance C <sub>1</sub> , C <sub>2</sub> of the values 10 $\mu$ F and 5 $\mu$ F respectively are connected in series. Evaluate the equivalent capacitance.	CO1	BTL3	Apply
16.	Two inductances L <sub>1</sub> =3mH and L <sub>2</sub> =6mH are connected in parallel. Analyze and calculate L <sub>eq</sub>	CO1	BTL3	Apply
17.	Two resistances when connected in series, the effective value of resistance are 100 Ohms. When connected in parallel the effective value is 24. Determine the value of resistance R1 and R2.	CO1	BTL3	Apply
18.	How much current flows through a conductor of resistance 20 Ohm when it is supplied with a potential difference of 200 V?	CO1	BTL4	Analyze
19.	A resistor of 3.6 $\Omega$ is connected in series with another resistor of 4.56 $\Omega$ . What resistance should be connected across 3.6 $\Omega$ resistor so that the total resistance of the circuit shall be 6 $\Omega$ ?	CO1	BTL4	Analyze
20.	How the series circuit is distinguished with parallel circuits?	CO1	BTL4	Analyze
21.	Point out the difference between DC Current with AC Current.	CO1	BTL4	Analyze
22.	Estimate the resultant resistance produced by the parallel connection of two resistors of 10 $\Omega$ and 30 $\Omega$ .	CO1	BTL4	Analyze
23.	For a purely resistive circuit excited by sinusoidal varying voltage, what are the phase angle and power factor?	CO1	BTL4	Analyze
24.	Generalize the expressions for mesh current equations in matrix Form.	CO1	BTL2	Understand
<b>PART – B</b>				
1.	Two resistors are connected in parallel and a voltage of 200 Volts is	CO1	BTL1	Remember

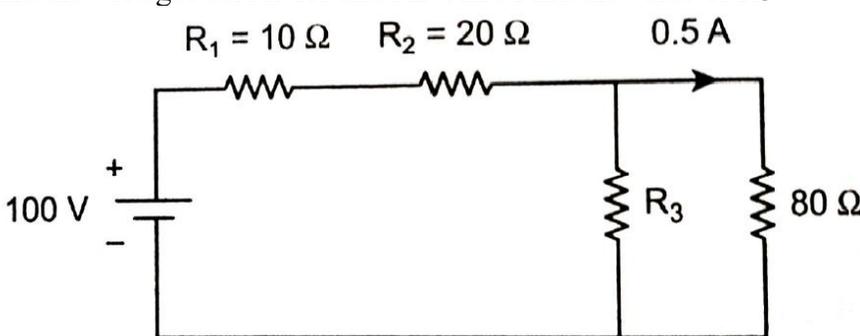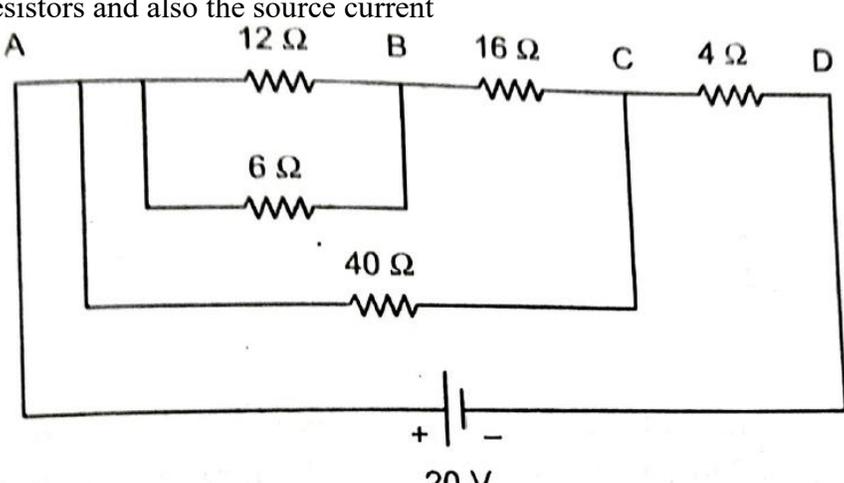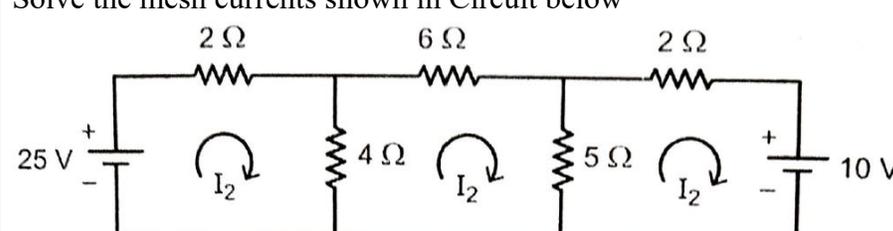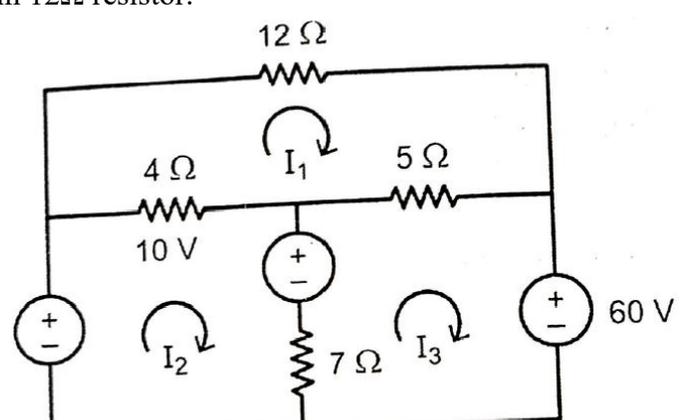	applied to the terminals. The total current taken is 25A and the power dissipated in one of the resistor is 1500W. What is the resistance of each element?			
2.	Three resistors of $6\Omega$ , $9\Omega$ and $15\Omega$ are connected in parallel to an 18V supply. Calculate (a) the current in each branch of the network, and supply current (b) total resistance of the network	CO1	BTL1	<b>Remember</b>
3.	Find the voltages across $R_1$ and $R_2$ . Also Find the value of $R_3$	CO1	BTL1	<b>Remember</b>
				
4.	Calculate the equivalent resistance of the following combination of resistors and also the source current	CO1	BTL1	<b>Remember</b>
				
5.	Solve the mesh currents shown in Circuit below	CO1	BTL2	<b>Understand</b>
				
6.	Analyze the circuit using Mesh current method and determine the current in $12\Omega$ resistor.	CO1	BTL2	<b>Understand</b>
				

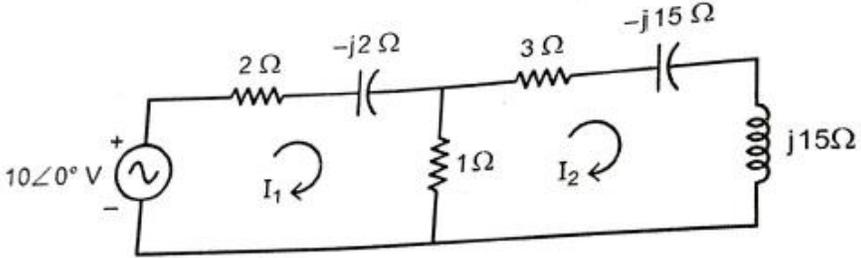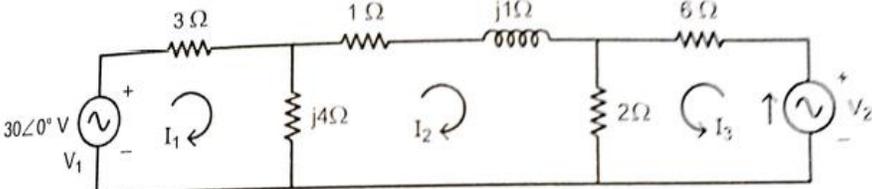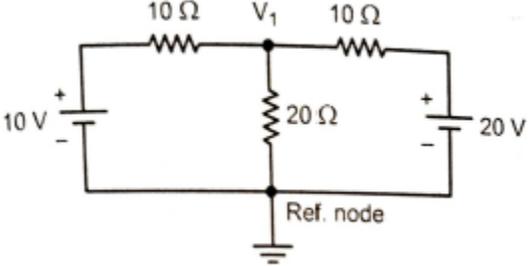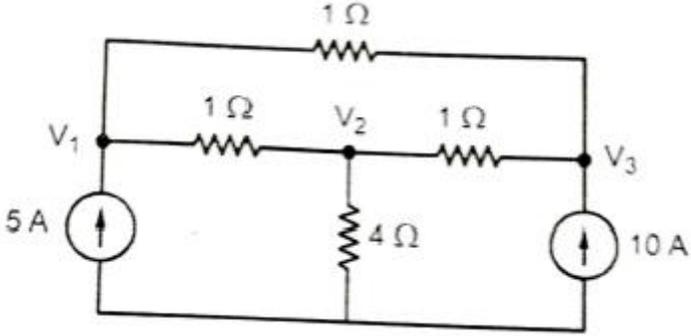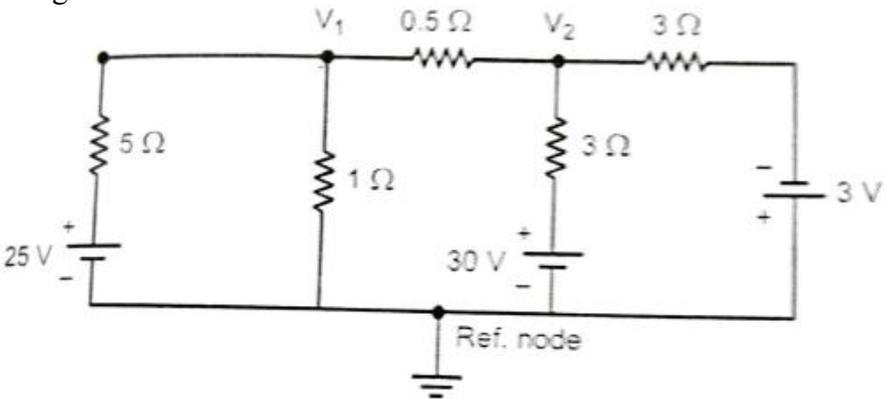
7.	<p>Apply the mesh current method and determine the current through the resistor of the network shown in Fig. below</p> 	CO1	BTL2	<b>Understand</b>
8.	<p>In the network shown below, find <math>V_2</math> such that the current in <math>(1 + j1) \Omega</math> branch is zero.</p> 	CO1	BTL2	<b>Understand</b>
9.	<p>Using Nodal analysis, determine the current in the <math>20 \Omega</math> resistor</p> 	CO1	BTL3	<b>Apply</b>
10.	<p>Find <math>V_1, V_2</math> and <math>V_3</math> by nodal method for the given circuit.</p> 	CO1	BTL3	<b>Apply</b>
11.	<p>Find the voltage of the nodes 1 and 2 in the network shown below by using nodal method.</p> 	CO1	BTL3	<b>Apply</b>
12.	<p>Calculate the current through the <math>4 \Omega</math> resistor using nodal analysis</p>	CO1	BTL3	<b>Apply</b>

	<p>technique</p>			
13.	A coil having a resistance of $6\ \Omega$ and an inductance of $0.03\text{H}$ is connected across a $100\text{V}$ , $50\text{Hz}$ supply. Calculate the current, phase angle between current and voltage, power factor and power.	CO1	BTL4	Analyze
14.	A coil when connected to $200\text{V}$ , $50\text{Hz}$ supply takes a current of $10\text{A}$ and dissipates $1200\text{W}$ . Find the resistance and inductance of the coil.	CO1	BTL4	Analyze
15.	A capacitor having a capacitance of $10\mu\text{F}$ is connected in series with a non-inductive resistance of $120\ \Omega$ across $100\text{V}$ , $50\text{Hz}$ supply. Calculate the current, power and the phase difference between current and supply voltage.	CO1	BTL4	Analyze
16.	A coil of resistance $10\ \Omega$ and an inductance of $0.1\text{H}$ is connected in series with a condenser of capacitance $150\mu\text{F}$ across a $200\text{V}$ , $50\text{Hz}$ supply. Calculate the inductive reactance of the coil, capacitive reactance, net reactance, current and power factor of the circuit.	CO1	BTL4	Analyze
17.	Calculate the current through $6\ \Omega$ resistor by kirchoff's Law.	CO1	BTL4	Analyze

## UNIT II - NETWORK REDUCTION & THEOREMS FOR DC AND AC CIRCUITS






**Network reduction: voltage and current division, source transformation – star delta conversion. Theorems – Superposition, Thevenin's and Norton's Theorem – Maximum power transfer theorem –Reciprocity Theorem – Millman's theorem.**

### PART – A

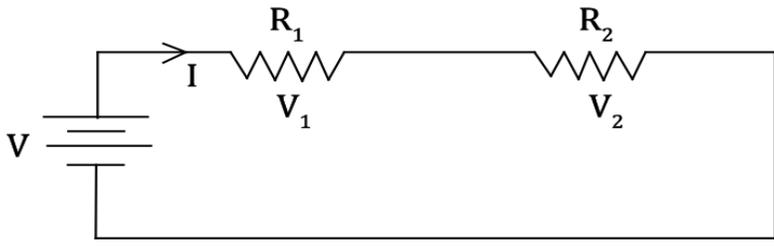Q.No	Questions	CO	BT Level	Competence
1.	Distinguish linear and nonlinear elements with suitable example for each. .	CO2	BTL1	Remember
2.	Define the term Electric network.	CO2	BTL1	Remember
3.	Illustrate the equivalent voltage source for a current source of 15A when connected in parallel with 5 ohm resistance	CO2	BTL1	Remember
4.	Given that the resistors $R_a$ , $R_b$ and $R_c$ are connected electrically in star. Formulate the equations for resistors in equivalent delta	CO2	BTL1	Remember
5.	Three resistors $R_{ab}$ , $R_{bc}$ and $R_{ca}$ are connected in delta. Re-write the expression for resistors in equivalent star.	CO2	BTL1	Remember
6.	Write the formulae for voltage division rule with suitable circuit.	CO2	BTL1	Remember
7.	Write the formulae for current division rule with suitable circuit.	CO2	BTL2	Understand
8.	Draw the circuit of a practical voltage source and its equivalent current source	CO2	BTL2	Understand
9.	For the given circuit, apply voltage division rule and Find the values of $V_1$ and $V_2$ .	CO2	BTL2	Understand
				
10.	Explain Thevenin's Theorem.	CO2	BTL2	Understand
11.	A load is connected to a network of the terminals to which load is connected in which $R_{th}=10$ Ohms and $V_{th}=40$ Volts. Calculate the maximum power supplied to the load.	CO2	BTL2	Understand
12.	State reciprocity theorem.	CO2	BTL3	Apply
13.	Is reciprocity theorem applied to the circuit having resistors, capacitors and diodes? Give your reason.	CO2	BTL3	Apply
14.	State Superposition theorem.	CO2	BTL3	Apply
15.	List out the applications of maximum power transfer theorem.	CO2	BTL3	Apply
16.	Distinguish between DC Current and AC Current.	CO2	BTL3	Apply
17.	What is the condition for maximum power transfer in DC and AC circuits?	CO2	BTL3	Apply
18.	A load is connected to a network of the terminals to which load is connected, $R_{th}=10$ ohms and $V_{th}=40$ Calculate the maximum power supplied to the load.	CO2	BTL4	Analyze
19.	State Millman's theorem.	CO2	BTL4	Analyze
20.	State Reciprocity theorem.	CO2	BTL4	Analyze

21.	Write the statement for Norton's theorem.	CO2	BTL4	Analyze
22.	Mention the different types of dependent source.	CO2	BTL4	Analyze
23.	What is the condition for maximum power transfer in DC Circuit?	CO2	BTL4	Analyze
24.	State Maximum power theorem.	CO2	BTL2	Understand

**PART – B**

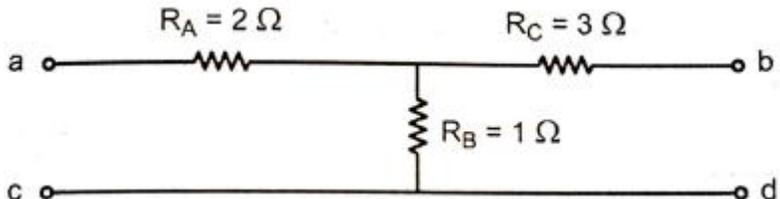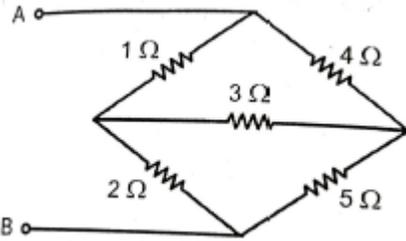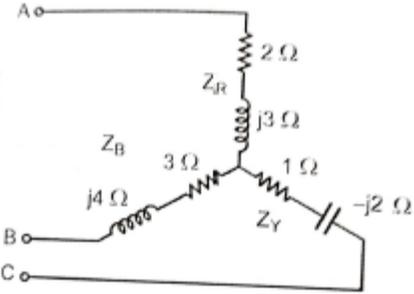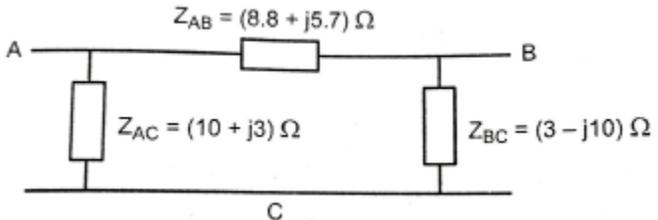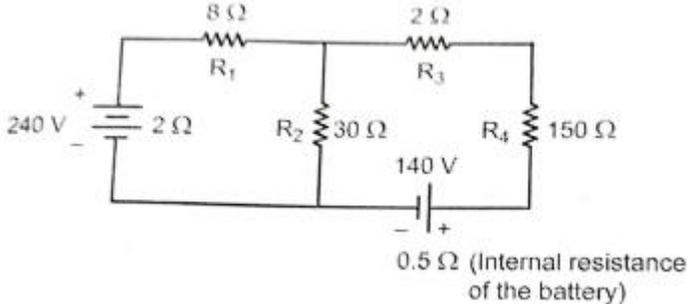1.	Obtain the delta connected equivalent for the star connected circuit shown below. 	CO2	BTL1	Remember
2.	Use the technique of delta-star conversion to find the equivalent resistance between A – B of the circuit shown. 	CO2	BTL1	Remember
3.	For the given ac circuit, obtain the delta network. 	CO2	BTL1	Remember
4.	Determine the star network for the given circuit. 	CO2	BTL1	Remember
5.	Find the current in 150Ω load resistor and the power consumed in it by the principle of superposition. 	CO2	BTL2	Understand
6.	Calculate the current in 4Ω using superposition theorem for the given	CO2	BTL2	Understand

	<p>circuit.</p>			
7.	<p>Illustrate superposition theorem for the given network.</p>	CO2	BTL2	<b>Understand</b>
8.	<p>Use Thevenin's Theorem to find the current through 5Ω resistance in the circuit diagram shown below.</p>	CO2	BTL3	<b>Apply</b>
9.	<p>Apply Thevenin's Theorem to determine the current through the 5Ω resistor.</p>	CO2	BTL3	<b>Apply</b>
10.	<p>Find the thevenin's equivalent for the given network.</p>	CO2	BTL3	<b>Apply</b>
11.	<p>With the help of Norton's Theorem, find the current through 6Ω resistor.</p>	CO2	BTL3	<b>Apply</b>
12.	<p>In the circuit shown below, find the value of adjustable resistor R for maximum power transfer to R. Also calculate the maximum power.</p>	CO2	BTL4	<b>Analyze</b>

13.	Verify reciprocity theorem for the circuit below.	CO2	BTL4	Analyze
14.	Find $I_3$ and prove the reciprocity theorem for the given circuit.	CO2	BTL4	Analyze
15.	For the circuit below, validate the reciprocity theorem.	CO2	BTL4	Analyze
16.	Determine the Norton's equivalent between the terminals AB.	CO2	BTL4	Analyze
17.	State and explain Millman's Theorem with necessary illustration?	CO2	BTL2	Understand

**UNIT III - TRANSIENT RESPONSE ANALYSIS**



**Transient response of RL, RC and RLC Circuits using Laplace transform for DC input and A.C. with sinusoidal input –Characterization of two port networks in terms of Z, Y and h parameters.**

**PART – A**

<b>Q.No</b>	<b>Questions</b>	<b>CO</b>	<b>BT Level</b>	<b>Competence</b>
1.	In a series RLC circuit, L=2H and C= 5μF. Calculate the value of R to give critical damping.	CO3	BTL1	<b>Remember</b>
2.	What is the time constant for series RL and RC circuits?	CO3	BTL1	<b>Remember</b>
3.	Distinguish between transient response and steady state response of a circuit.	CO3	BTL1	<b>Remember</b>
4.	Generalize the frequency response of series RLC circuit.	CO3	BTL1	<b>Remember</b>
5.	Define the term 'Time Constant'. And write formulae for R <sub>L</sub> , R <sub>C</sub> Circuit.	CO3	BTL1	<b>Remember</b>
6.	Write Integral-differential equation of RLC Circuit with the supply voltage E.	CO3	BTL1	<b>Remember</b>
7.	Classify the periodic inputs.	CO3	BTL2	<b>Understand</b>
8.	Define (i) transient response (ii) Exponential decay response. Write the formulae for RL Transient Response	CO3	BTL2	<b>Understand</b>
9.	Distinguish between free and forced response.	CO3	BTL2	<b>Understand</b>
10.	Illustrate the time constant of RL Circuit having the resistance R=10 Ohm and L=0.1mH.	CO3	BTL2	<b>Understand</b>
11.	Define the terms (i) Transient Time (ii) Time Constant (iii) Natural response (iv) Steady state response.	CO3	BTL2	<b>Understand</b>
12.	Develop an equivalent circuit for inductor and capacitor at t=0+ when there is no initial energy.	CO3	BTL3	<b>Apply</b>
13.	A DC Voltage of 100 Volts is applied to Series RL Circuit with R=25 Ohm. Calculate the value of current in which time constant is twice.	CO3	BTL3	<b>Apply</b>
14.	Analyze the current given by $I(t) = 5 - 4e^{-20t}$	CO3	BTL3	<b>Apply</b>
15.	Define time constant for RL circuit. Draw the transient current characteristics.	CO3	BTL3	<b>Apply</b>
16.	Sketch the transient response of I, V <sub>R</sub> , V <sub>L</sub> in Series RL Circuit.	CO3	BTL3	<b>Apply</b>
17.	Describe about under damping.	CO3	BTL3	<b>Apply</b>
18.	Draw the phasor diagram for a pure inductor	CO3	BTL4	<b>Analyze</b>
19.	State the expression for capacitive reactance and its unit.	CO3	BTL4	<b>Analyze</b>
20.	State the relationship between frequency and period.	CO3	BTL4	<b>Analyze</b>
21.	Calculate the time constant for series RLC circuit?	CO3	BTL4	<b>Analyze</b>
22.	Let a RL circuits has 50Ω and 1mH elements and free of source but, the inductor has initial current of 1 mA at time t=0's. Find the voltage across the resistor at time t=□.	CO3	BTL4	<b>Analyze</b>
23.	Find the time constant of RL Circuit with R=100 Ohms and L=20 mH?	CO3	BTL4	<b>Analyze</b>
24.	Define instantaneous value of a.c voltage.	CO3	BTL2	<b>Understand</b>

**PART – B**

1.	Derive the expression for transient response of RL series circuit excited by DC voltage.	CO3	BTL2	<b>Understand</b>
2.	Derive the expression for transient response of RC series circuit excited by DC voltage.	CO3	BTL2	<b>Understand</b>
3.	In the given circuit, find the expression for the transient current and the initial rate of growth of the transient current.	CO3	BTL3	<b>Apply</b>
4.	In the following circuit, the switch S is in position 1 for a long time and brought to position 2 at time $t=0$ . Determine the circuit current.	CO3	BTL3	<b>Apply</b>
5.	Find how long it takes after the key is closed before the total current from the supply reaches 25mA, when $V = 10V$ , $R_1 = 500\Omega$ , $R_2 = 700\Omega$ and $C = 100\mu F$ .	CO3	BTL3	<b>Apply</b>
6.	A series RLC circuit with $R = 5\Omega$ , $L = 0.1H$ and $C = 500\mu F$ has a DC voltage of 100V applied at $t=0$ through a switch. Find the resulting current transient.	CO3	BTL3	<b>Apply</b>
7.	A sinusoidal voltage of $10\sin 100t$ is connected in series with a switch and $R=10\Omega$ and $L=0.1H$ . If the switch is closed at $t=0$ , Determine the transient current $i(t)$ .	CO3	BTL1	<b>Remember</b>
8.	In the circuit shown, determine the transient current after switch is	CO3	BTL2	<b>Understand</b>

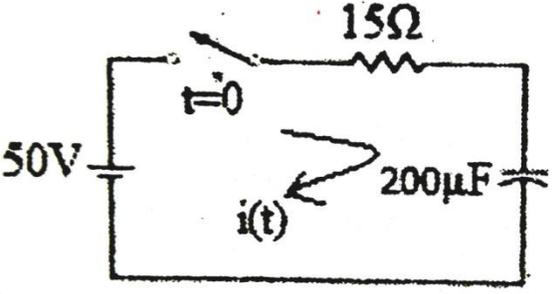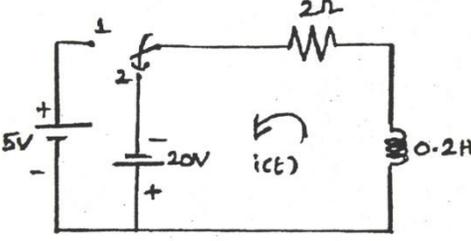	<p>closed at time <math>t=0</math>, given that an initial charge of <math>100\mu\text{C}</math> is stored in the capacitor. Derive the necessary equations.</p> 			
9.	<p>In the RL circuit shown in fig, the switch is closed to position 1 at <math>t=0</math>. After <math>t=100\text{ms}</math>, the switch is changed to position 2. Find <math>i(t)</math> and sketch the transient.</p> 	CO3	BTL2	<b>Understand</b>
10.	Derive the h- parameters for a two port network.	CO3	BTL1	<b>Remember</b>
11.	Illustrate the derivation of Z – parameters for a two port network.	CO3	BTL1	<b>Remember</b>
12.	With the help of necessary equations , explain how to express h-parameters in terms of Y-parameters	CO3	BTL4	<b>Analyze</b>
13.	The Z – parameters of a two port network are $Z_{11} = 40\Omega$ , $Z_{22} = 50\Omega$ , $Z_{12} = Z_{21} = 20\Omega$ . Find the equivalent T – network..	CO3	BTL4	<b>Analyze</b>
14.	<p>For a two port network, measurements are made and observed as below:</p> <p>(i) With output terminal pair open, a voltage of <math>100\angle 0^\circ</math> through the input port resulted in <math>I_1 = 20\angle 0^\circ</math> Amperes and <math>V_2 = 25\angle 0^\circ</math> Volts</p> <p>(ii) With input terminal pair open, the same voltage applied to the output terminal pair resulted in <math>I_2 = 20\angle 0^\circ</math> Amperes and <math>V_1 = 40\angle 0^\circ</math> Volts.</p> <p>Find the Z – parameters and write the loop equations</p>	CO3	BTL4	<b>Analyze</b>
15.	The Z – parameters of a two port network are $Z_{11} = 25\Omega$ , $Z_{22} = 40\Omega$ , $Z_{12} = Z_{21} = 10\Omega$ . Find the Y – Parameters.	CO3	BTL4	<b>Analyze</b>
16.	For a two port network, Y – parameters are : $Y_{11} = 0.1\text{mho}$ , $Y_{22} = 0.05\text{mho}$ , $Y_{12} = Y_{21} = -0.02\text{mho}$ . Calculate the Z – parameters for the same network.	CO3	BTL4	<b>Analyze</b>
17.	Tabulate the conversion expression between Z, Y and h parameters.	CO3	BTL1	<b>Remember</b>

**UNIT IV – THREE PHASE CIRCUITS**


**Three phase balanced / unbalanced voltage sources –analysis of three phase 3- wire and 4-wire circuits with star and delta connected loads, balanced & unbalanced –phasor diagram of voltages and currents –power and power factor measurements in three phase circuits**

**PART – A**

<b>Q.No</b>	<b>Questions</b>	<b>CO</b>	<b>BT Level</b>	<b>Competence</b>
1.	Point out the advantages of 3-phase system over 1phase system.	CO4	BTL 4	Analyze
2.	Assess the various methods of power measurement in 3Φ circuits	CO4	BTL 5	Evaluate
3.	Define (i) Average value (ii) RMS value (iii) Crest factor (iv) Form factor.	CO4	BTL 1	Remember
4.	Evaluate the voltage across Y and B in a 3 Φ balanced delta system with voltage across R and Y is 400∠00 V. Assume RYB phase	CO4	BTL 5	Evaluate
5.	Distinguish between unbalanced source and unbalanced load.	CO4	BTL 2	Understand
6.	A 3Φ 400V supply is given to a balanced star connected load of impedance 8+j6 ohms in each branch. Formulate the line current.	CO4	BTL 6	Create
7.	Define power factor in terms of impedance and power components.	CO4	BTL 2	Understand
8.	Define form factor. What is the value of Form factor for sinusoidal signal.	CO4	BTL 3	Apply
9.	Calculate the power factor if $V(t)=V_m \sin \omega t$ and $I(t)=I_m \sin(\omega t-45^\circ)$ .	CO4	BTL 3	Apply
10.	Evaluate the formulae for two watt meter method for the measurement of power.	CO4	BTL 4	Analyze
11.	Compare star and delta connected system.	CO4	BTL 4	Analyze
12.	Define average value and RMS value.	CO4	BTL 1	Remember
13.	Define power factor.	CO4	BTL 1	Remember
14.	Describe the terms (i) Line voltage (ii) Line current .	CO4	BTL 2	Understand
15.	Differentiate active and reactive power in electrical circuits.	CO4	BTL 2	Understand
16.	How do you differentiate Power and Energy in Electrical Circuits?	CO4	BTL 1	Remember
17.	Draw the phasor diagram of voltages derived from a 3phase source.	CO4	BTL 6	Create
18.	Distinguish between balanced supply and unbalanced load.	CO4	BTL 2	Understand
19.	In a reactive circuit, the current leads the voltage by angle 45°. Find whether the resultant reactive is either inductive or capacitive and power factor.	CO4	BTL 3	Apply
20.	Write the expression for determining reactive and apparent power in a three phase circuit.	CO4	BTL 1	Remember

21.	Define the terms : Phase and Phase difference.	CO4	BTL 1	Remember
22.	What are the three types of power in AC Circuits ?	CO4	BTL 2	Understand
23.	Define Phasor diagram	CO4	BTL 1	Remember
24.	What is the phase sequence of a three phase system?	CO4	BTL 2	Understand
<b>PART – B</b>				
1.	A balanced three phase load consists of a 6 $\Omega$ resistor and 8 $\Omega$ resistor (inductive) in each phase. The supply is 230V, 3-phase, 50 Hz. Find (i) the phase current (ii) line current (iii) the total power. Assume the load to be connected in star.	CO4	BTL3	Apply
2.	A symmetrical 3-phase, 400V system supplies a balanced delta connected load. The current in each branch is 20A and phase angle 60°C (lag). Calculate the line current and total power.	CO4	BTL 4	Analyze
3.	(i) A 3-phase balanced delta-connected load of (4+j8) $\Omega$ is connected across a 400V,3-phase supply. Determine the phase currents and line currents. Assume the RYB phase sequence. Also calculate the value of the power drawn by the load. (ii) Three equal inductors connected in star, take 5kW at 0.7pf when connected to a 400V,50Hz, three phases ,three wire supply. Calculate the line currents (1) if one of the inductors is disconnected (2) if one of the inductors is short circuited.	CO4	BTL 4	Analyze
4.	Discuss in detail about the three phase 3-wire circuits with (i) Star connected balanced loads (ii) Delta balanced Loads.	CO4	BTL 1	Remember
5.	A delta connected balanced load is supplied from a 3 phase 400V supply. The line current is 20A. Total power taken by load is 10000W. Calculate the impedance in each branch, the line current, power factor and total power consumed if the same load is connected in star.	CO4	BTL3	Apply
6.	Explain three phase power measurement by 2 wattmeter method for star and delta connected load and determine the power equation and draw phasor diagram.	CO4	BTL2	Understand
7.	The two wattmeter produces wattmeter readings $P_1=1560W$ and $P_2=2100W$ When connected to delta connected load. If the line voltage is 220V, Calculate (1)the per phase average power (2) total reactive power. (3) Power factor (4) the phasor impedance. Is the impedance inductive or Capacitive?	CO4	BTL3	Apply
8.	Explain the following Three Phase Loads for Balanced and Unbalanced Loads for (i) Star Connected Loads (ii)Delta Connected Loads. (i) Determine the line current, power factor and total power when a 3- phase 400V supply is given to a balanced load of impedance(8+j6) $\Omega$ in each branch is connected instar.	CO4	BTL2	Understand
9.	Discuss the method of measuring power in a three phase system with balanced and unbalanced load conditions.	CO4	BTL 1	Remember
10.	An unbalanced star – connected load is supplied from a 3 phase 440V, symmetrical system. Determine the line currents and the power output to the circuit shown in Figure. Assume RYB sequences. Take phase voltages $V_{RN}$	CO4	BTL 4	Analyze

as reference in the supply side.

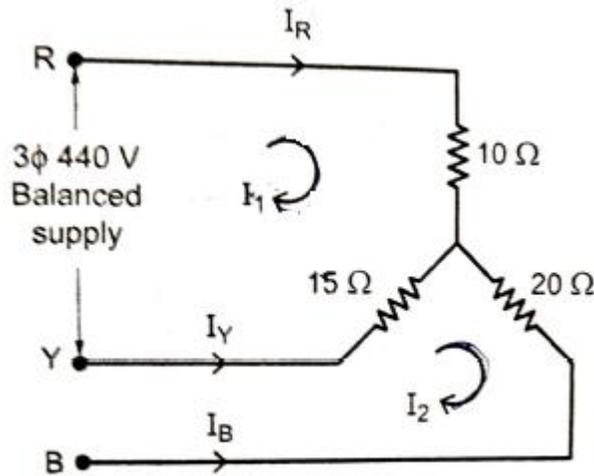

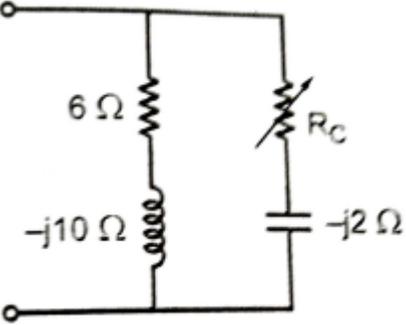
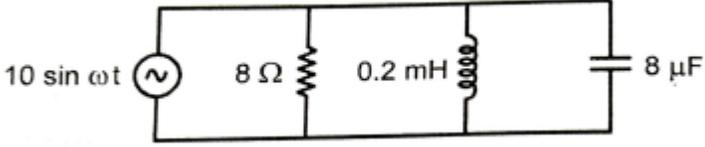
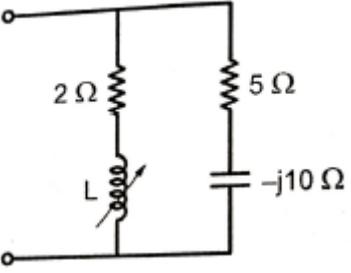
11.	Explain the measurement of power in 3 phase circuit using one wattmeter method.	CO4	BTL2	<b>Understand</b>
12.	(i)Mention the Merits of Three Phase System compare with Single Phase System. (ii) Explain the following connection wiring for Three Phase Systems (a) Interconnection of Winding (b) Star Connection (c) Delta Connection with Phasor Diagram.	CO4	BTL 1	<b>Remember</b>
13.	Three impedances $Z_1 = 20 \angle 30^\circ$ , $Z_2 = 40 \angle 60^\circ$ , $Z_3 = 10 \angle -90^\circ$ ohms are delta connected to a 400 V, three phase system. Determine the phase currents and total power consumed by the load.	CO4	BTL 4	<b>Analyze</b>
14.	Derive the relationship between the phase voltage and line voltage of a 3 phase star connected balanced system.	CO4	BTL2	<b>Understand</b>
15.	Two wattmeter are used to measure power in a three phase load. The wattmeter readings are 400W and -35W. Calculate total active power, power factor and reactive power.	CO4	BTL3	<b>Apply</b>
16.	Explain the power and power factor measuring in the three phase by two wattmeter method.	CO4	BTL1	<b>Remember</b>
17.	Two wattmeter are connected to measure the power in a 3 phase 3 wire balanced loads. Determine the total power and power factor if the two wattmeter read (i) 1000W each, both positive and (ii) 1000W w each of opposite sign.	CO4	BTL 4	<b>Analyze</b>



**UNIT V – RESONANCE AND COUPLED CIRCUITS**




**Series and parallel resonance –frequency response – Quality factor and Bandwidth – Self and mutual inductance – Coefficient of coupling Analysis of coupled circuits– Single Tuned circuits.**

**PART – A**

<b>Q.No</b>	<b>Questions</b>	<b>CO</b>	<b>BT Level</b>	<b>Competence</b>
1.	Write the expression for coefficient of coupling.	CO5	BTL1	<b>Remember</b>
2.	What is meant by Resonance?	CO5	BTL1	<b>Remember</b>
3.	What is meant by anti-resonance circuit? Illustrate the frequency response curve for Parallel RLC Circuit?	CO5	BTL1	<b>Remember</b>
4.	Write the expression for resonant frequency for series RLC Circuit.	CO5	BTL1	<b>Remember</b>
5.	Express the term tuned circuits. Mention the different tuned circuits.	CO5	BTL1	<b>Remember</b>
6.	Draw the series resonant circuit.	CO5	BTL1	<b>Remember</b>
7.	Illustrate the expression of maximum energy stored in (i) Inductor (ii) Capacitor.	CO5	BTL2	<b>Understand</b>
8.	Discuss about the quality factor of a series resonant circuit.	CO5	BTL2	<b>Understand</b>
9.	Define the term Coefficient of coupling.	CO5	BTL2	<b>Understand</b>
10.	Illustrate the quality factor of a coil for the series resonant circuit consisting of R= 10 ohm, L= 0.1 henry and C= 10 microfarad.	CO5	BTL2	<b>Understand</b>
11.	Define bandwidth of a resonant circuit.	CO5	BTL2	<b>Understand</b>
12.	Describe the expression which relates the self and mutual inductance.	CO5	BTL3	<b>Apply</b>
13.	Examine the maximum possible mutual inductance of two inductively coupled circuits with self inductance $L_1 = 16 \text{ H}$ and $L_2 = 4 \text{ H}$ .	CO5	BTL3	<b>Apply</b>
14.	Define the term Mutual inductance (ii) Coefficient of coupling.	CO5	BTL3	<b>Apply</b>
15.	What is an antiresonance circuit? Create the frequency response of RLC Parallel Circuit.	CO5	BTL3	<b>Apply</b>
16.	Illustrate the expression for effective inductance of two series connected magnetically coupled coils.	CO5	BTL3	<b>Apply</b>
17.	Two coupled coils with $L_1 = 0.02 \text{ H}$ , $L_2 = 0.01 \text{ H}$ and $K = 0.5$ are connected in series aiding arrangement. Obtain the equivalent inductance.	CO5	BTL3	<b>Apply</b>
18.	Define self-inductance and mutual inductance of a coil.	CO5	BTL4	<b>Analyze</b>
19.	What is meant by single tuned coupled circuits?	CO5	BTL4	<b>Analyze</b>
20.	Define quality factor Q of a coil.	CO5	BTL4	<b>Analyze</b>
21.	Two identical coils with $L = 0.03 \text{ H}$ have a coupling coefficient of $K = 0.8$ . Find the mutual inductance and the equivalent inductance with the coils connected in series opposing mode.	CO5	BTL4	<b>Analyze</b>
22.	What is meant by tuned circuits ? List some applications of tuned circuits.	CO5	BTL4	<b>Analyze</b>
23.	A resistor of 50 Ohm an inductor of 0.02 H and a capacitor of 5 $\mu\text{F}$ are connected in series. Find the resonant frequency and power factor at resonance.	CO5	BTL4	<b>Analyze</b>

24.	Compare the properties of series and parallel resonant circuits.	CO5	BTL2	<b>Understand</b>
<b>PART – B</b>				
1.	Explain briefly about the concept of parallel resonance.	CO5	BTL1	<b>Remember</b>
2.	A series circuit with $R = 10\text{ohms}$ , $L = 10\text{mH}$ and $C = 1\mu\text{F}$ has an applied voltage of $200\text{V}$ at resonant frequency. Calculate the (i) Resonant frequency, Quality factor and bandwidth (ii) Current in the circuit and voltage across the elements of resonance	CO5	BTL3	<b>Apply</b>
3.	Determine the value of $R_c$ in the network shown in figure to yield resonance? 	CO5	BTL3	<b>Apply</b>
4.	For a Series RLC Circuit i) Derive the condition for resonance ii) Explain the frequency response and Obtain quality factor and bandwidth.	CO5	BTL1	<b>Remember</b>
5.	In the parallel RLC circuit in Figure, Calculate resonant frequency, bandwidth and Q factor 	CO5	BTL4	<b>Analyze</b>
6.	The circuit shown in figure is resonant at a frequency of $\omega = 5000\text{ rad/sec}$ . Find the value of $L$ . 	CO5	BTL4	<b>Analyze</b>
7.	For the circuit shown in figure, determine the value of $C$ which it resonates when $f = 100\text{Hz}$ .	CO5	BTL3	<b>Apply</b>

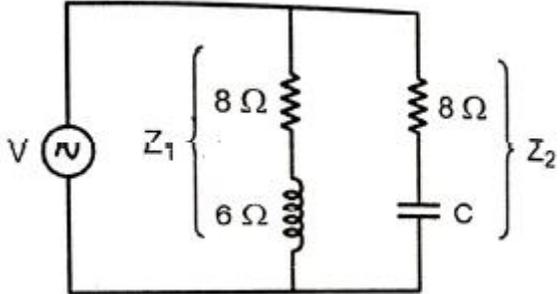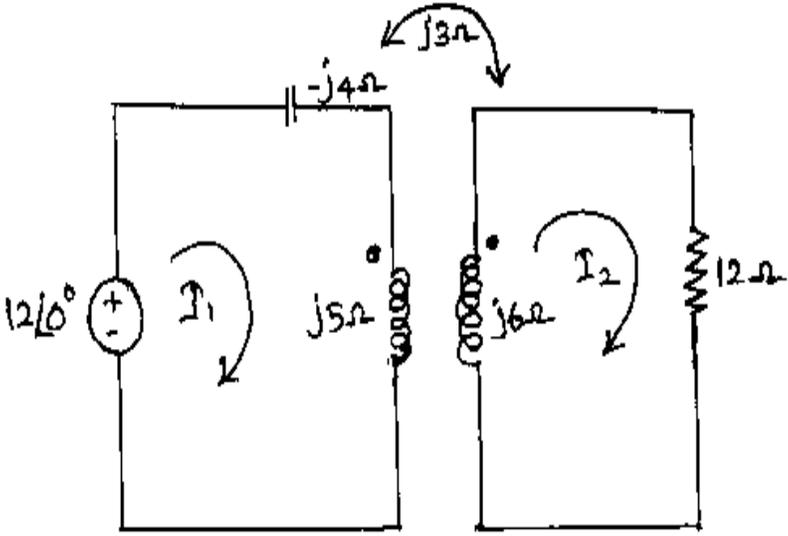				
8.	<p>Two inductively coupled coils have self inductance <math>L_1 = 30\text{mH}</math> and <math>L_2 = 100\text{mH}</math>. If the coefficient of coupling is 0.5</p> <p>(i) Find the value of mutual inductance between the coils</p> <p>(ii) What is the maximum possible mutual inductance?</p>	CO5	BTL3	<b>Apply</b>
9.	<p>Two identical coupled coils in series has an equivalent inductance of <math>0.080\text{H}</math> and <math>0.0354\text{H}</math> when connected in series aiding and series opposing respectively. Find the values of the inductance, mutual inductance and the coefficient of coupling.</p>	CO5	BTL4	<b>Analyze</b>
10.	<p>Draw the conductively coupled equivalent circuit for the given circuit in fig. and also find the voltage drop across <math>12\Omega</math> resistor.</p> 	CO5	BTL2	<b>Understand</b>
11.	<p>The number of turns in two coupled coils are 500 turns and 1500 turns respectively. When 5A current flows in coil 1, the total flux in this coil is <math>0.6 \times 10^{-3}</math> wb and flux linking in second coil is <math>0.3 \times 10^{-3}</math> wb. Determine <math>L_1</math>, <math>L_2</math>, <math>M</math> and <math>K</math>.</p>	CO5	BTL2	<b>Understand</b>
12.	<p>For the circuit shown in Fig. determine the voltage ratio <math>V_1/V_2</math>, which will make the current <math>I_1</math> equal to zero.</p>	CO5	BTL4	<b>Analyze</b>

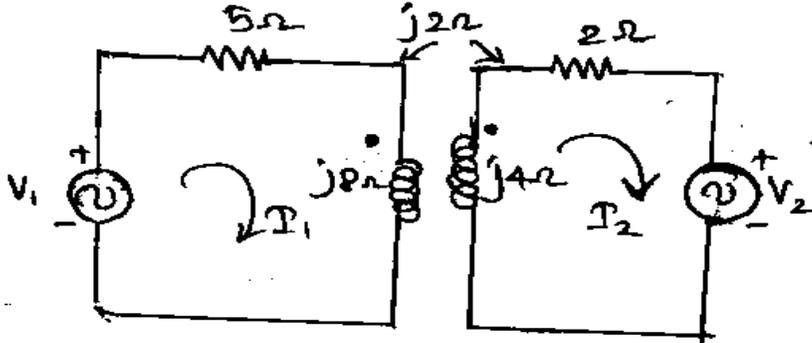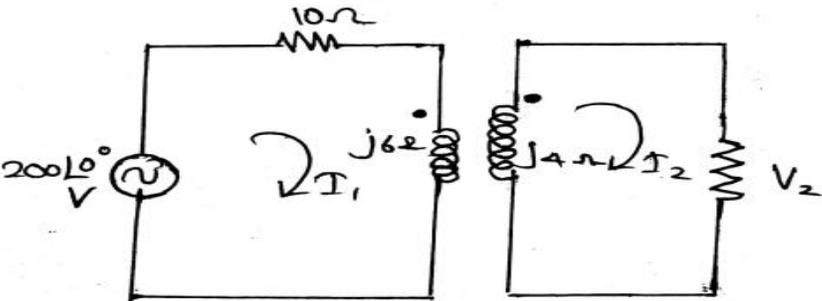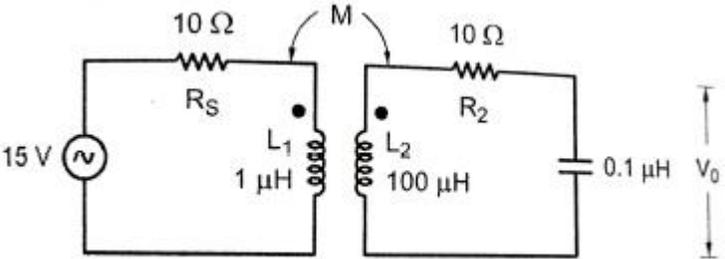				
13.	<p>A coil having an inductance of 100mH is magnetically coupled to another coil having an inductance of 900mH. The coefficient of coupling between the coils is 0.45. Calculate the equivalent inductance if the two coils are connected in 1) Series opposing 2) Parallel opposing.</p>	CO5	BTL1	<b>Remember</b>
14.		CO5	BTL2	<b>Understand</b>
15.	<p>Two coupled coils of self inductance <math>L_1 = 2\text{H}</math> and <math>L_2 = 4\text{H}</math> are coupled in (i) series aiding (ii) series opposing (iii) parallel aiding (iv) parallel opposing. If the mutual inductance is 0.5H, Find the equivalent inductance in each case.</p>	CO5	BTL4	<b>Analyze</b>
16.	<p>Express the term self inductance and mutual inductance for the coupled circuits.</p>	CO5	BTL1	<b>Remember</b>
17.		CO5	BTL2	<b>Understand</b>